 




OF THE
DEPARTMENT OF
INFORMATION ENGINEERING



UNIVERSITÀ
DEGLI STUDI
DI PADOVA

Digital Systems

Exercises on Combinational Circuits

Marta Bagatin, marta.bagatin@unipd.it

Degree Course in Information Engineering
Academic Year 2023-2024

Example 3-17: Mux Implementation of 4-Variable Function


- Implement the following Boolean function through a mux with a 3-bit selection signal

$$F(A, B, C, D) = \sum m(1, 3, 4, 11, 12, 13, 14, 15)$$

Example 3-17: Mux Implementation of 4-Variable Function

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


- a) We find the truth table of the function
- b) We use a mux with 3 selection inputs (8-to-1 line mux)

 

Example 3-17: Mux Implementation of 4-Variable Function

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


- a) We find the truth table of the function
- b) We use a mux with 3 selection inputs (8-to-1 line mux)
- c) We connect the 3 most significant among the 4 inputs A, B, C, D to the mux selection inputs (pay attention to the order!)

 

Example 3-17: Mux Implementation of 4-Variable Function

A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = \bar{D}$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	


- a) We find the truth table of the function
- b) We use a mux with 3 selection inputs (8-to-1 line mux)
- c) We connect the 3 most significant among the 4 inputs A, B, C, D to the mux selection inputs (pay attention to the order!)
- d) We appropriately set the value of the mux data inputs (value fixing) based on the truth table

 

 Example 3-18: BCD-to-Seven Segments Decoder

- **Specifications:** Design a combinational circuit that accepts a decimal digit in BCD as an input and produces the appropriate outputs for the LEDs (Light Emitting Diodes) segments of the display for that decimal digit.

The circuit needs to control the correct illumination of the 7 segments to represent the input digit. For the unused input combinations (1010-1111) the display needs to be off



Names of the 7 segments



Representation of the 9 BCD digits on the display

Example 3-18: BCD-to-Seven Segments Decoder


- **Specifications:** Design a combinational circuit that accepts a decimal digit in BCD as an input and produces the appropriate outputs for the LEDs (Light Emitting Diodes) segments of the display for that decimal digit.

The circuit needs to control the correct illumination of the 7 segments to represent the input digit

Inputs and Outputs:

- 4 inputs: A B C D (represent the ten BCD digits)
- 7 outputs: a b c d e f g (control of the 7 segments)

=> The outputs of the circuit select the corresponding segment in the display, to correctly represent the input digit (output = '0': LED turned off, output= '1': LED turned on)

 

Example 3-18: BCD-to-Seven Segments Decoder

• Truth table:

BCD Input				Seven-Segment Decoder						
A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
All other inputs				0	0	0	0	0	0	0

Input:
BCD code of
digits 0 to 9

Output = '0': LED
segment off
Output = '1': LED
segment on

Combinations 1010-1111:
display off

0 1 2 3 4 5 6 7 8 9

Example 3-18: BCD-to-Seven Segments Decoder

- **Boolean function determination:**

- 1st implementation: with logic gates

- Optimization: 7 Karnaugh-maps, one for each output (a, b, c, d, e, f, g)
 - Independent implementation of these 7 functions requires 27 AND gates and 7 OR gates

$$a = \overline{A}C + \overline{A}BD + \overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}$$

$$b = \overline{A}\overline{B} + \overline{A}\overline{C}\overline{D} + \overline{A}CD + A\overline{B}\overline{C}$$

$$c = \overline{A}B + \overline{A}D + \overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}$$

$$d = \overline{A}C\overline{D} + \overline{A}\overline{B}C + \overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C} + \overline{A}B\overline{C}D$$

$$e = \overline{A}C\overline{D} + \overline{B}\overline{C}\overline{D}$$

$$f = \overline{A}B\overline{C} + \overline{A}\overline{C}\overline{D} + \overline{A}B\overline{D} + A\overline{B}\overline{C}$$

$$g = \overline{A}C\overline{D} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C}$$

Example 3-18: BCD-to-Seven Segments Decoder

- Boolean function determination:**

1st implementation: with logic gates

- Optimization: 7 Karnaugh-maps, one for each output (a, b, c, d, e, f, g)
- Independent implementation of these 7 functions requires 27 AND gates and 7 OR gates
- By sharing the common product terms among the different outputs, the number of AND gates can be reduced to 15

$$\begin{aligned}
 a &= \bar{A}C + \bar{A}BD + \boxed{\bar{B}\bar{C}\bar{D}} + \textcircled{A\bar{B}\bar{C}} \\
 b &= \bar{A}\bar{B} + \underline{\bar{A}\bar{C}\bar{D}} + \bar{A}CD + \textcircled{A\bar{B}\bar{C}} \\
 c &= \bar{A}B + \bar{A}D + \boxed{\bar{B}\bar{C}\bar{D}} + \textcircled{A\bar{B}\bar{C}} \\
 d &= \textcolor{violet}{\diamond} \bar{A}\bar{C}\bar{D} + \bar{A}\bar{B}C + \boxed{\bar{B}\bar{C}\bar{D}} + \textcircled{A\bar{B}\bar{C}} + \bar{A}B\bar{C}D \\
 e &= \textcolor{violet}{\diamond} \bar{A}\bar{C}\bar{D} + \boxed{\bar{B}\bar{C}\bar{D}} \\
 f &= \underline{\bar{A}B\bar{C}} + \underline{\bar{A}\bar{C}\bar{D}} + \bar{A}B\bar{D} + \textcircled{A\bar{B}\bar{C}} \\
 g &= \textcolor{violet}{\diamond} \bar{A}\bar{C}\bar{D} + \bar{A}\bar{B}C + \underline{\bar{A}B\bar{C}} + \textcircled{A\bar{B}\bar{C}}
 \end{aligned}$$

Example 3-18: BCD-to-Seven Segments Decoder

2nd implementation: with decoder

- We use a 4-to-16 decoder to generate all the minterms corresponding to the 4 inputs of the circuit
- Then we connect the minterms of the functions to 7 OR gates (one for each output)

BCD Input				Seven-Segment Decoder						
A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
All other inputs				0	0	0	0	0	0	0

$$a(A, B, C, D) = \Sigma m(0, 2, 3, 5, 6, 7, 8, 9)$$

$$b(A, B, C, D) = \Sigma m(0, 1, 2, 3, 4, 7, 8, 9)$$

$$c(A, B, C, D) = \Sigma m(0, 1, 3, 4, 5, 6, 7, 8, 9)$$

$$d(A, B, C, D) = \Sigma m(0, 2, 3, 5, 6, 8, 9)$$

$$e(A, B, C, D) = \Sigma m(0, 2, 6, 8)$$

$$f(A, B, C, D) = \Sigma m(0, 4, 5, 6, 8, 9)$$

$$g(A, B, C, D) = \Sigma m(2, 3, 4, 5, 6, 8, 9)$$

Example 3-18: BCD-to-Seven Segments Decoder

3rd implementation: with multiplexer

- Seven line mux 8-to-1 (one for each output)
 - Selection inputs $S_2 S_1 S_0$ connected to A, B, C (pay attention to the order!)
 - Data inputs $I_0, I_1, I_2, \dots, I_7$ connected appropriately to D, \bar{D} , 0, 1

BCD Input				Seven-Segment Decoder						
A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
All other inputs				0	0	0	0	0	0	0

Select Inputs $S_2 S_1 S_0$	Multiplexer Data Inputs for Each Output Function						
	a	b	c	d	e	f	g
000	\bar{D}	1	1	\bar{D}	\bar{D}	\bar{D}	0
001	1	1	D	1	\bar{D}	0	1
010	D	\bar{D}	1	D	0	1	1
011	1	D	1	\bar{D}	\bar{D}	\bar{D}	\bar{D}
100	1	1	1	1	\bar{D}	1	1
101	0	0	0	0	0	0	0
110	0	0	0	0	0	0	0
111	0	0	0	0	0	0	0

Example 3-18: BCD-to-Seven Segments Decoder

3rd implementation: with multiplexer

- Seven line mux 8-to-1 (one for each output)
 - Selection inputs $S_2 S_1 S_0$ connected to A, B, C (pay attention to the order!)
 - Data inputs $I_0, I_1, I_2, \dots, I_7$ connected appropriately to D, \bar{D} , 0, 1

BCD Input				Seven-Segment Decoder						
A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	0
0	0	0	1	1	0	1	1	0	0	0
0	0	1	0	0	1	1	0	1	1	0
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	0	1	1	0	0	1
0	1	0	1	1	1	0	1	1	0	1
0	1	1	0	0	1	0	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	0	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
All other inputs				0	0	0	0	0	0	0


Select Inputs $S_2 S_1 S_0$	Multiplexer Data Inputs for Each Output Function						
	a	b	c	d	e	f	g
000	\bar{D}	1	1	\bar{D}	\bar{D}	\bar{D}	0
001	1	1	D	1	\bar{D}	0	1
010	D	\bar{D}	1	D	0	1	1
011	1	D	1	\bar{D}	\bar{D}	\bar{D}	\bar{D}
100	1	1	1	1	\bar{D}	1	1
101	0	0	0	0	0	0	0
110	0	0	0	0	0	0	0
111	0	0	0	0	0	0	0

Prime Circuit

- Write the VHDL code describing the following circuit
 - Input (4 bit): input
 - Output (1 bit): isPrime, '1' if input is prime, '0' otherwise

in the following ways:

 
- 1) Structural description
- 2) Dataflow description
- 3) Behavioral description



- Write a testbench to check the circuit functionality and simulate it with EDA Playground

Prime Circuit

 As a first step we find the logic circuit (optimized with K-maps):




Prime Circuit

1) Structural-dataflow description (1/2)

```
library IEEE;  
use IEEE.std_logic_1164.all;
```

```
entity Prime is  
    port (input: in std_logic_vector (3 downto 0);  
          isPrime: out std_logic);  
end Prime;
```

```
architecture implStruct of Prime is  
    signal a1, a2, a3, a4, n1, n2, n3: std_logic;  
    begin  
        AND1: entity work.andGate(andImpl) port map(a1, n3, input(0));  
        AND2: entity work.andGate(andImpl) port map(a2, input(2), n1, input(0));  
        AND3: entity work.andGate(andImpl) port map(a3, n2, input(1), input(0));  
        AND4: entity work.andGate(andImpl) port map(a4, n3, n2, input(1));  
        n3 <= NOT input(3);  
        n2 <= NOT input(2);  
        n1 <= NOT input(1);  
        isPrime <= a1 OR a2 OR a3 OR a4;  
    end implStruct;
```

 

AND component with 3 inputs, set to '1' by default (defined in the next slide)

Prime Circuit

1) Structural-dataflow description (2/2)

```
library IEEE;  
use IEEE.std_logic_1164.all;  
  
entity andGate is  
    port (y: out std_logic;  
          a, b, c: in std_logic: = '1');  
end andGate;  
  
architecture andImpl of andGate is  
    begin  
        y <= a and b and c;  
    end andImpl;
```

Prime Circuit

2) Dataflow description

```
library IEEE;  
use IEEE.std_logic_1164.all;
```


```
entity Prime is  
    port (input: in std_logic_vector (3 downto 0);  
          isPrime: out std_logic);
```

```
end Prime;
```

```
architecture implLogic of Prime is  
    begin
```

```
    isPrime <= (input(0) AND NOT(input(3))) OR  
               (input(1) AND NOT (input(2)) AND NOT(input(3))) OR  
               (input(0) AND NOT (input(1)) AND input(2)) OR  
               (input(0) AND input(1) AND NOT (input(2)));
```

```
end implLogic;
```

 

Prime Circuit

3.a) Behavioral description with **case** statement

```
library IEEE;  
use IEEE.std_logic_1164.all;
```

```
entity Prime is  
    port (input: in std_logic_vector (3 downto 0);  
          isPrime: out std_logic);  
end Prime;
```

```
architecture implCase of Prime is  
    begin  
        process(input) begin  
            case input is  
                when x"1" | x"2" | x"3" | x"5" | x"7" | x"b" | x"d" => isPrime <= '1';  
                when others => isPrime <= '0';  
            end case;  
        end process;  
    end implCase;
```



x to indicate
hexadecimal
numbers

Case Statement: Parallel Logic

Syntax of case statement:

```
case expression is
  when choice1 => {statements}
  when choice2 => {statements}
  when others => {statements}
end case;
```

- The case statement is a sequential statement similar to combinational statement "with-select" and it **needs to appear inside a process**
- Allows us to specify the value of a logic function for all the combinations of the inputs
- **All possible choices need to be covered** (as "with select") and the various **choices cannot overlap**
- The statement "null" can be used to perform no action under specific conditions
- **All inputs must appear in the sensitivity list of a process to generate combinational logic**

Prime Circuit

3.b) Behavioral description with **if** statement

```
entity Prime is
  port (input: in std_logic_vector (3 downto 0);
        isPrime: out std_logic);
end Prime;
```

```
architecture implIf of Prime is
begin
  process (input) begin
    if input = 4d"1" then isPrime <= '1';
    elsif input = 4d"2" then isPrime <= '1';
    elsif input = 4d"3" then isPrime <= '1';
    elsif input = 4d"5" then isPrime <= '1';
    elsif input = 4d"7" then isPrime <= '1';
    elsif input = 4d"11" then isPrime <= '1';
    elsif input = 4d"13" then isPrime <= '1';
    else isPrime <= '0';
    end if;
  end process;
end implIf;
```

4d: 4-bit
decimal

If Statement: Priority Logic

Syntax for if statement:

```
if condition1 then
    {sequential_statement1}
elsif condition2 then
    {sequential_statement2}
else
    {sequential_statement3}
end if;
```

- The if statement is a sequential statement similar to combinational statement "when-else" and it must appear **inside a process**
- Evaluates each condition in order, i.e. it generates a priority structure (similar to concurrent statement "when-else ")
- Caution: All choices need to be covered to implement combinational logic using if-else statement
- **All inputs must appear in the sensitivity list of a process to generate combinational logic**

Exercise 3-55: Arithmetic Operations

- **Perform the following arithmetic operations between the following signed numbers in 2s complement representation.** Then verify the results and indicate whether overflow occurs for each computation
 - a) $110001 + 011101$
 - b) $0110111 + 0101111$
 - c) $00000111 - 11110100$
 - d) $0110111 - 0101111$

Exercise 3-55: Arithmetic Operations

a) **110001 + 011101**

Carry: **1**10001

$$\begin{array}{r} 110001 + \\ 011101 \\ \hline 001110 \end{array}$$

Verification:

$$-15 + 29 = +14$$

NOTE:

- There is no overflow since the carry bits in the n and $n-1$ positions are equal
- Carry out in the sign bit position is 1 (and it must be discarded)

Exercise 3-55: Arithmetic Operations

b) **0110111 + 0101111**

Carry: 0111111

$$\begin{array}{r} 0110111 + \\ 0101111 \\ \hline 01100110 \end{array}$$

Verification:

$$+55 + 47 = + 102$$

NOTE:

- **There is overflow** since the carry bits in the n and n-1 positions are different: we need to consider the carry-out in the sign bit position as the sign bit of the result
- The carry out in the sign bit position is zero

Exercise 3-55: Arithmetic Operations

c) **0000 0111 - 1111 0100**

For subtraction with signed numbers, we sum the 2's complement of the subtrahend to the minuend

Carry: 0001 1000

$$\begin{array}{r} 0000\ 0111\ + \\ 0000\ 1100 \\ \hline 0001\ 0011 \end{array}$$

Verification:

$$+7 - (-12) = +19$$

NOTE:

- There is no overflow

Exercise 3-55: Arithmetic Operations

d) 0110111 - 0101111

Carry: 1110111
 0110111 +
 1010001

 0001000

Verification:
 $+55 - (+47) = +8$

NOTE:

- There is no overflow
- There is a carry out in the sign bit position (and it must be discarded)

Exercise

- Write the VHDL code describing a 2-to-4 decoder with:
 - Dataflow architecture
 - Behavioral architecture using the 'when else' statement
 - Behavioral architecture using the 'with select' statement
- Realize a VHDL testbench to simulate the correct functionality of the circuit with all the input combinations using one of the architectures above

Exercise

- Write the VHDL code describing a 4-to-1 multiplexer with:
 - Dataflow architecture
 - Behavioral architecture using the 'if' statement
 - Behavioral architecture using the 'case' statement
- Realize a VHDL testbench to simulate the correct functionality of the circuit with all the input combinations using one of the architectures above

Disclaimer

Figures from *Logic and Computer Design Fundamentals*,
Fifth Edition, GE Mano | Kime| Martin

© 2016 Pearson Education, Ltd