 




OF THE
DEPARTMENT OF
INFORMATION ENGINEERING



UNIVERSITÀ
DEGLI STUDI
DI PADOVA

Digital Systems

Basic Sequential Blocks in VHDL: Latch and Flip-flop

Marta Bagatin, marta.bagatin@unipd.it

Degree Course in Information Engineering

Academic Year 2023-2024

Purpose of the Lesson

- Describe in VHDL and simulate the **basic sequential elements**
 - SR Latch with control input
 - D Latch
 - D Flip-flop with asynchronous reset
 - D Flip-flop with synchronous reset

Process Statement: Review

- Within a process, the statements **are executed sequentially**, i.e. one after the other, in the order in which they are written and in an infinitesimal time (in the absence of specific explicit commands, such as «wait»)
- **All processes within an architecture run simultaneously**
- The value of the signals assigned within a process is updated only when the process is suspended (because all statements within the process have been executed or because there is a «wait» instruction)
- A process may have a **sensitivity list**, containing the signals to which the process is sensitive: the process is **activated** when there is a **change** in one or more signals in the sensitivity list
 - To describe a combinational circuit, the sensitivity list must contain all the inputs of the circuit
 - A testbench typically uses processes without a sensitivity list: such processes are activated immediately at the start of the simulation

Process Statement: Review

Syntax for the process statement:

```
[processName:] process [(<sensitivity_list>)]  
begin  
    <sequential_instruction>  
end process;
```



- The **sensitivity list** contains the signals to which change the process is sensitive. If the sensitivity list is empty (e.g. in a testbench), the process runs continuously
- A name can be assigned to the process (before the keyword `process` and it must be followed by ":")

Latch

- SR Latch with control input
- D Latch

SR Latch with Control Input: Review

  - The **control input C** acts as an enable signal
 - $C = 0$: latch not enabled, it keeps the previous state
 - $C = 1$: latch enabled, it works as an SR type latch
 - $S = 1, R = 0$: set state: $Q = 1, \bar{Q} = 0$
 - $S = 0, R = 1$: reset state: $Q = 0, \bar{Q} = 1$
 - $S = 0, R = 0$: memory state
 - $S = 1, R = 1$: forbidden state: $Q = 1, \bar{Q} = 1$





SR Latch with Enable: VHDL (Dataflow)

```
library IEEE;
use IEEE.std_logic_1164.all;

entity SRLatch is
    port(S, R, C : in std_logic;
         Q, Q_n : out std_logic);
end SRLatch;

  -- Dataflow architecture
architecture dataflow of SRLatch is
    signal S_n, R_n: std_logic;
begin
    S_n <= S nand C;
    R_n <= R nand C;
    Q <= S_n nand Q_n;
    Q_n <= R_n nand Q;
end dataflow;
```



SR Latch with Enable: VHDL (Behavioral)

```
architecture behavioral of SRlatch is
  signal SR: std_logic_vector (1 downto 0);
begin
  SR <= S & R;
  process (SR, C) begin
    if (C = '1') then
      case (SR) is
        when "00" => -- S = R = 0: MEMORY
          null;


        when "01" => -- S = 0, R = 1: RESET
          Q <= '0';
          Q_n <= '1';

        when "10" => -- S = 1, R = 0: SET
          Q <= '1';
          Q_n <= '0';

        when "11" => -- S = R = 1: FORBIDDEN
          Q <= '1';
          Q_n <= '1';

        when others =>
          Q <= 'X';
          Q_n <= 'X';
        end case;
      end if;
    end process;
end behavioral;
```

 «process» with S,
R, and C in the
sensitivity list




«if-else» statement
without specifying
all cases (C = '0')
generates memory,
i.e. sequential logic!

SR Latch with Enable: VHDL Testbench (1/2)

```
library IEEE;
use IEEE.std_logic_1164.all;


entity testbench is
end testbench;

architecture test of testbench is
    signal setReset: std_logic_vector(1 downto 0);
    signal control, output, output_n: std_logic;
begin
    DUT: entity work.Srlatch (behavioral) port map( setReset(1), setReset(0), control, output, output_n);
    process begin
        setReset <= "10";
        control<='1';
        wait for 2 ns;
        setReset <= "00";
        wait for 5 ns;
        setReset <= "01";
        wait for 6 ns;
        setReset <= "00";
        wait for 4 ns;
        setReset <= "10";
        wait for 6 ns;
        setReset <= "01";
        wait for 5 ns;
        setReset <= "00";
```

 


SR Latch with Enable: VHDL Testbench (2/2)
 
```
wait for 6 ns;  
setReset <= "11";  
wait for 5 ns;  
setReset <= "01";  
wait for 0.1 ns;  
setReset <= "00";  
wait for 8 ns;  
control<='0';  
wait for 4 ns;  
setReset <= "00";  
wait for 5 ns;  
setReset <= "01";  
wait for 6 ns;  
setReset <= "00";  
wait for 2 ns;  
wait;  
end process;  
end test;
```




 SR Latch with Enable Simulation: Time Diagram




C = 1: latch enabled
S = 1, R = 0: set
S = 0, R = 1: reset
S = 0, R = 0: memory
S = 1, R = 1: forbidden

C = 0: latch disabled

 


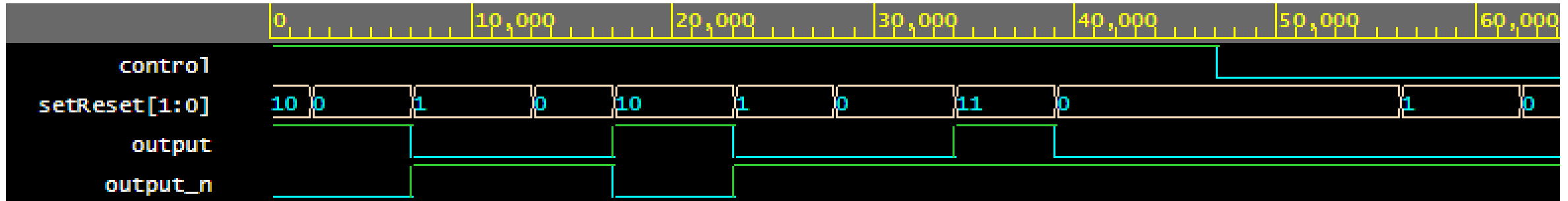SR Latch with Enable Simulation: Time Diagram




C = 1: latch enabled
S = 1, R = 0: set
S = 0, R = 1: reset
S = 0, R = 0: memory
S = 1, R = 1: forbidden

C = 0: latch disabled

 

D Latch: Review

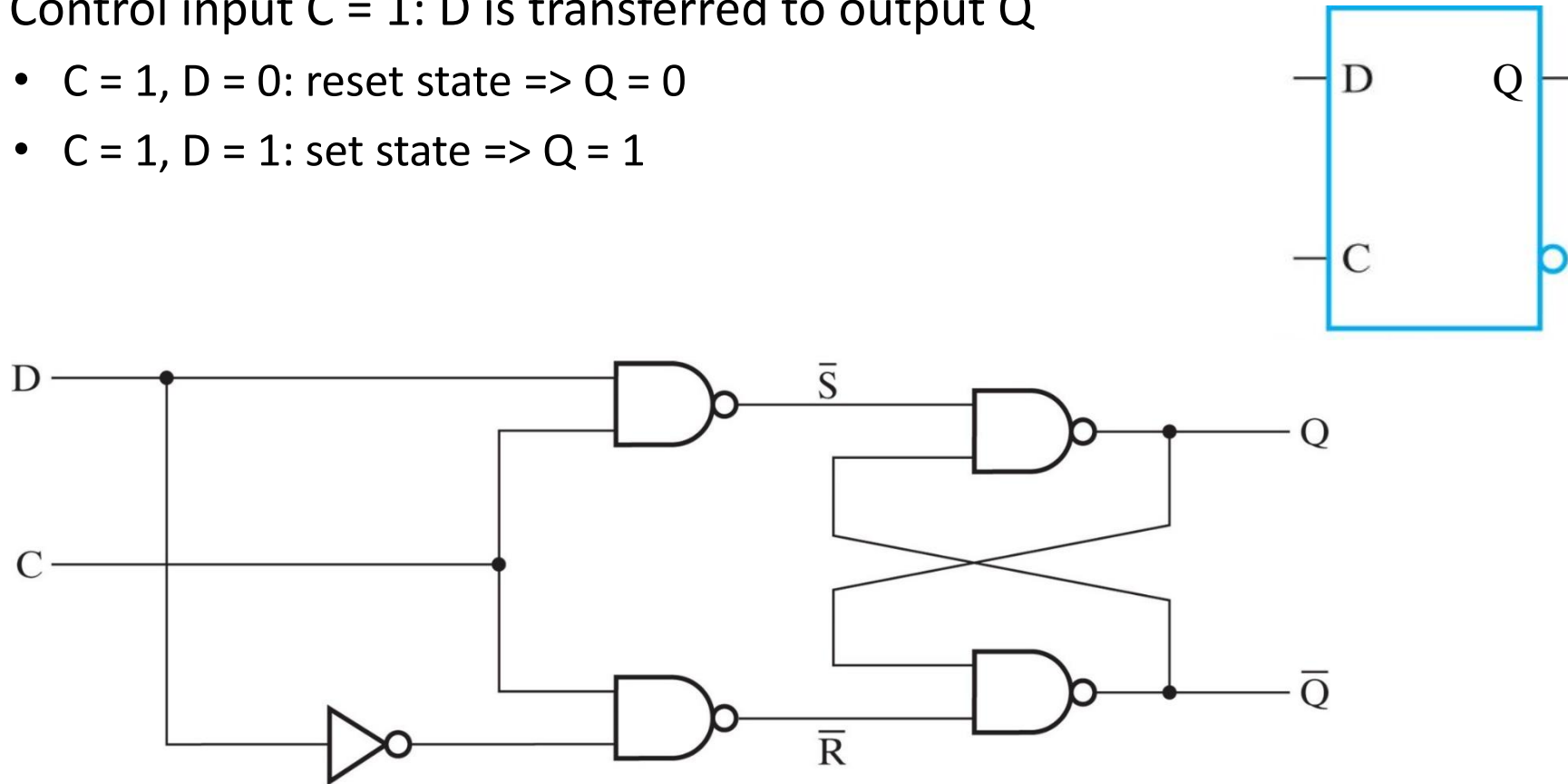- The D latch **avoids the problem of the forbidden state**, having a single data input
 - Control input $C = 0$: the circuit maintains the previous state (memory)
 - Control input $C = 1$: D is transferred to output Q
 - $C = 1, D = 0$: reset state $\Rightarrow Q = 0$
 - $C = 1, D = 1$: set state $\Rightarrow Q = 1$




D Latch: VHDL Design (Behavioral)

```
library IEEE;
use IEEE.std_logic_1164.all;

entity Dlatch is
    port (D, C : in std_logic;
          Q, Q_n : out std_logic);
end Dlatch;

 -- behavioral architecture
architecture Dlatch_arch of Dlatch is
begin
    process (D, C)
    begin
        if (C = '1') then
            Q <= D;
            Q_n <= not D;
        end if;
    end process;
end Dlatch_arch;
```



C = 0: keeps the previous state

C = 1: D is transferred to output Q

C = 1, D = 0: reset state => Q = 0


C = 1, D = 1: set state => Q = 1

D Latch: VHDL Testbench


```
library IEEE;
use IEEE.std_logic_1164.all;

entity testbench is
end testbench;

architecture test of testbench is
    signal data, control, output, output_n : std_logic;
begin
    DUT: entity work.Dlatch port map (data, control, output, output_n);
    process begin
        data <= '0';
        control <= '1';
        wait for 5 ns;
        data <= '1';
        wait for 5 ns;
        data <= '0';
        wait for 3 ns;
        data <= '1';
        wait for 4 ns;
        data <= '0';
        wait for 4 ns;
        control <= '0';
        wait for 3 ns;
        data <= '1';
        wait for 5 ns;
        data <= '0';
        wait;
    end process;
end test;
```

 

D Latch Simulation: Time Diagram

 


C = 1: D is transferred to output Q


C = 1, D = 0: reset state \Rightarrow Q = 0

C = 1, D = 1: set state \Rightarrow Q = 1

C = 0: keeps the previous state

 

D Latch Simulation: Time Diagram

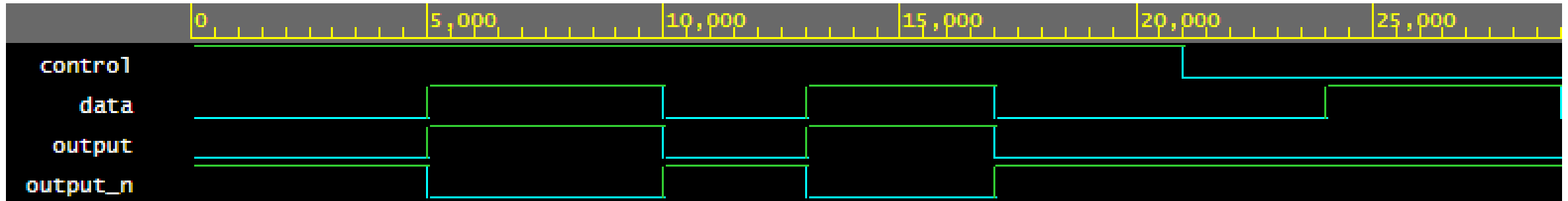


C = 1: D is transferred to output Q

C = 1, D = 0: reset state \Rightarrow Q = 0

C = 1, D = 1: set state \Rightarrow Q = 1

C = 0: keeps the previous state

 


D Flip-flops



- With asynchronous reset
- With synchronous reset

Flip-flop D: Review

 
- A positive-edge-triggered (or negative-edge-triggered) D flip-flop consists of two latches connected in cascade, driven by complementary control signals
 - At each rising (or falling) edge of the clock, the last value of D sampled by the master is transferred to the slave, e.g. to the flip-flop output Q
 - At all other instants of time, the previous state is maintained



PET-D-Flip-flop
Logic diagram
and symbol

 
 


NET-D-Flip-flop
Logic diagram
and symbol

 

D Flip-flop with Reset

  
- **Asynchronous reset:** the reset signal is asynchronous with respect to the clock, i.e. reset can arrive at any time
- **Synchronous reset:** the reset signal is synchronized with the clock, i.e. reset can only arrive at the clock edges (positive- or negative-edge-triggered FF). Therefore, synchronous reset **requires a clock trigger to be effective**



D-Flip flop with Asynchronous Reset: VHDL Design

```
library IEEE;
use IEEE.std_logic_1164.all;

 entity dff is
    port (CLK, RST, D: in std_logic;
          Q: out std_logic);
end dff;
-- behavioral architecture
architecture dff_as of dff is
begin
    process (RST, CLK)
    begin
        if (RST = '1') then
            Q <= '0';
        elsif (CLK'event and CLK = '1') then
            Q <= D;
        end if;
    end process;
end dff_as;
```




Reset is not synchronized with the clock: it can arrive at any time

D-Flip flop with Asynchronous Reset: VHDL Design

```
library IEEE;
use IEEE.std_logic_1164.all;

 entity dff is
    port (CLK, RST, D: in std_logic;
          Q: out std_logic);
end dff;
-- behavioral architecture
architecture dff_as of dff is
begin
    process (RST, CLK)
    begin
        if (RST = '1') then
            Q <= '0';
        elsif (CLK'event and CLK = '1') then
            Q <= D;
        end if;
    end process;
end dff_as;
```



The process is activated at the change of at least one between **CLK** and **RESET**


CLK'event is 1 whenever CLK changes. This boolean variable ANDed with «CLK = '1'» indicates a clock positive edge. "event" is an attribute of the clock signal

AT RESET: output becomes 0 (no matter the clock value)
AT CLK POSITIVE EDGE: output becomes D

D-Flip flop with Synchronous Reset: VHDL Design

```
library ieee;
use ieee.std_logic_1164.all;

 entity dff is
    port (CLK, RST, D: in std_logic;
          Q: out std_logic);
end dff;
-- behavioral architecture
architecture dff_sync of dff is
begin
    process (CLK)
    begin
        if (CLK'event and CLK = '1') then
            if (RST = '1') then
                Q <= '0';
            else
                Q <= D;
            end if;
        end if;
    end process;
end dff_sync;
```




Reset is synchronized with the clock: it can arrive only at the active clock edges

D-Flip flop with Synchronous Reset: VHDL Design

```
library ieee;
use ieee.std_logic_1164.all;

 entity dff is
    port (CLK, RST, D: in std_logic;
          Q: out std_logic);
end dff;
-- behavioral architecture
architecture dff_sync of dff is
begin
    process (CLK)
    begin
        if (CLK'event and CLK = '1') then
            if (RST = '1') then
                Q <= '0';
            else
                Q <= D;
            end if;
        end if;
    end process;
end dff_sync;
```



Only **CLK** signal is present in the sensitivity list

The **RESET** does no longer dominate the clock, it can only occur in correspondence of the rising edge

Simulation of Synchronous Sequential Logic



- It is necessary that **changes in the inputs occur far enough from the active clock edge** (e.g. during the falling edge in case of PET D-FF). In this way, combinational logic has the time to calculate the next state and the output before the next active clock edge
- We will implement the testbench with **two processes**, working in parallel:
 - 1) The first process **generates the clock**. This process is never explicitly stopped and runs continuously, ensuring that the clock keeps oscillating
 - 2) The second process **generates the sequence of input signals**, including the reset, with proper synchronization, for example at the falling edges of the clock. This process is stopped with the command `"std.env.stop"`, which ends the simulation

D-Flip-flop with Asynchronous Reset: Testbench (1/2)

```
library IEEE;
use IEEE.std_logic_1164.all;

entity test_dff is
end test_dff;

  architecture test of test_dff is
  signal clk, rst, input, output: std_logic;
begin
  DUT: entity work.dff (dff_as) port map (clk, rst, input, output);
  generate_clock: process
  begin
    clk <= '1';
    wait for 5 ns;
    clk <= '0';
    wait for 5 ns;
  end process;
```





Process to **generate the clock** (square wave with 10 ns period)



D-Flip-flop with Asynchronous Reset: Testbench (2/2)

```
apply_inputs: process
begin
    rst <= '0';
    input <= '0';
    wait for 15 ns;
    input <= '1';
    wait for 10 ns;
    rst <= '1';
    wait for 20 ns;
    rst <= '0';
    wait for 10 ns;
    input <= '0';
    wait for 10 ns;
    input <= '1';
    std.env.stop;
end process;
endtest;
```

  Process to **change the inputs** at the falling edge of the clock





  D-Flip-flop with Asynchronous Reset: Simulation



D-Flip-flop with Asynchronous Reset: Simulation

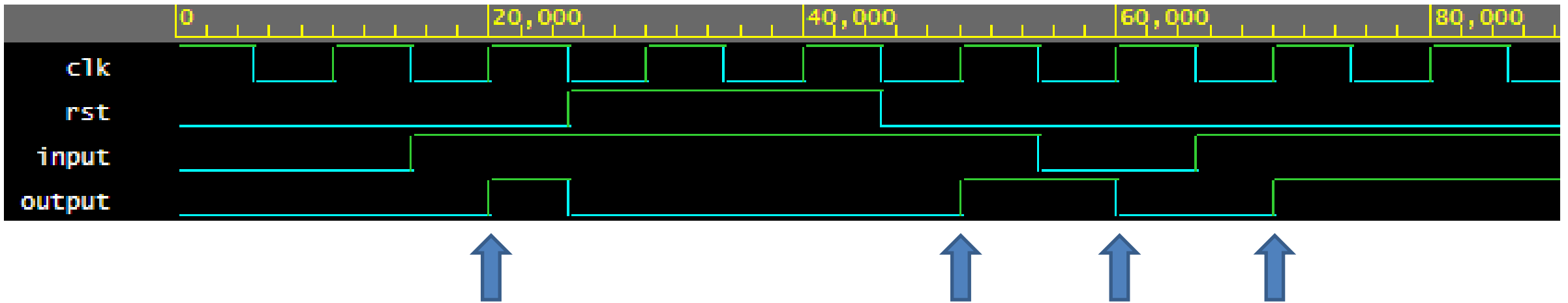 When reset = 1 (at any time, not necessarily at clock edges): the output becomes 0



When reset is zero: at the clock rising edges, the output follows the input

D-Flip-flop with Synchronous Reset: Testbench (1/2)

```
library IEEE;  
use IEEE.std_logic_1164.all;
```

```
entity test_dff is  
end test_dff;
```

```
architecture test of test_dff is  
  signal clk, rst, input, output: std_logic;  
begin
```

```
  DUT: entity work.dff (dff_sync) port map (clk, rst, input, output);
```

```
  generate_clock: process
```

```
  begin
```


```
    clk <= '1';
```

```
    wait for 5 ns;
```


```
    clk <= '0';
```

```
    wait for 5 ns;
```

```
  end process;
```

 


 
Process to
generate a **clock**
with period 10 ns





D-Flip-flop with Synchronous Reset: Testbench (2/2)

```
apply_inputs: process
begin
  rst <= '0';
  input <= '0';
  wait for 15 ns;
  input <= '1';
  wait for 10 ns;
  rst <= '1';
  wait for 10 ns;
  rst <= '0';
  wait for 10 ns;
  input <= '0';
  std.env.stop;
end process;
end test;
```

  
Process to **change the inputs and reset** at the falling edge of the clock



  
D-Flip-flop with Synchronous Reset: Simulation



 D-Flip-flop with Synchronous Reset: Simulation



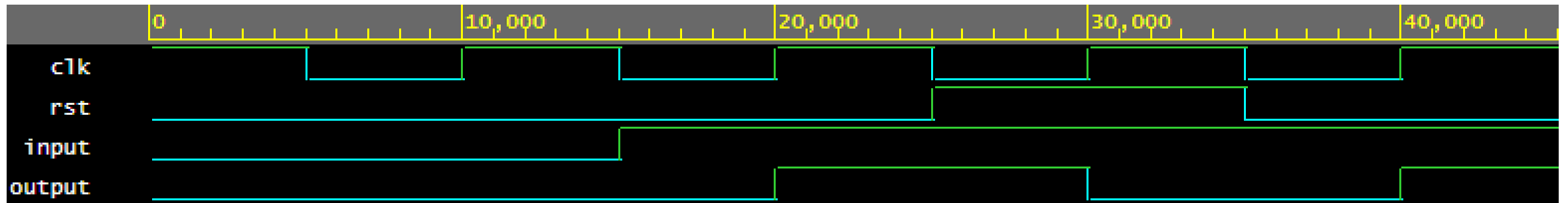Reset is asserted => the output goes to 0 at the next rising edge of the clock



If reset is 0: at the rising edges of the clock, the output follows the input

Disclaimer

Figures from *Logic and Computer Design Fundamentals*,
Fifth Edition, GE Mano |Kime| Martin

© 2016 Pearson Education, Ltd