

Memory – Part B

Types of memories, memory management

Gloria Beraldo (gloria.beraldo@unipd.it)


Department of Information Engineering, University of Padova

Topics:

- Types of memories
- RAM, SRAM, DRAM e SDRAM
- Array of memories SRAM
- Addressing, timing, refresh of the memories DRAM

Book Reference:

- Chapter 7

 

SRAM: Static Random Access Memory

- SR Latch as model of a cell SRAM


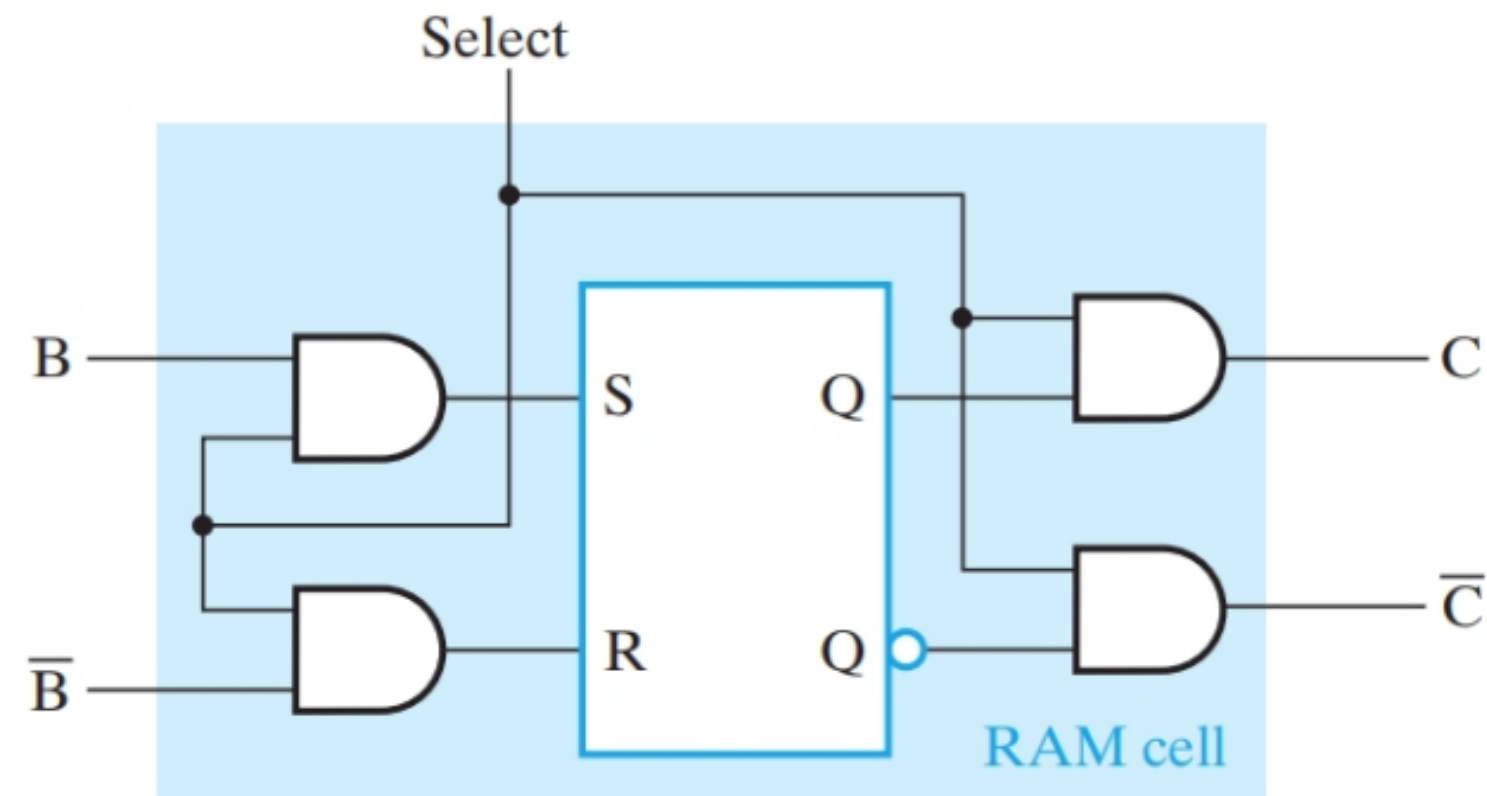


FIGURE 7-4
Static RAM Cell

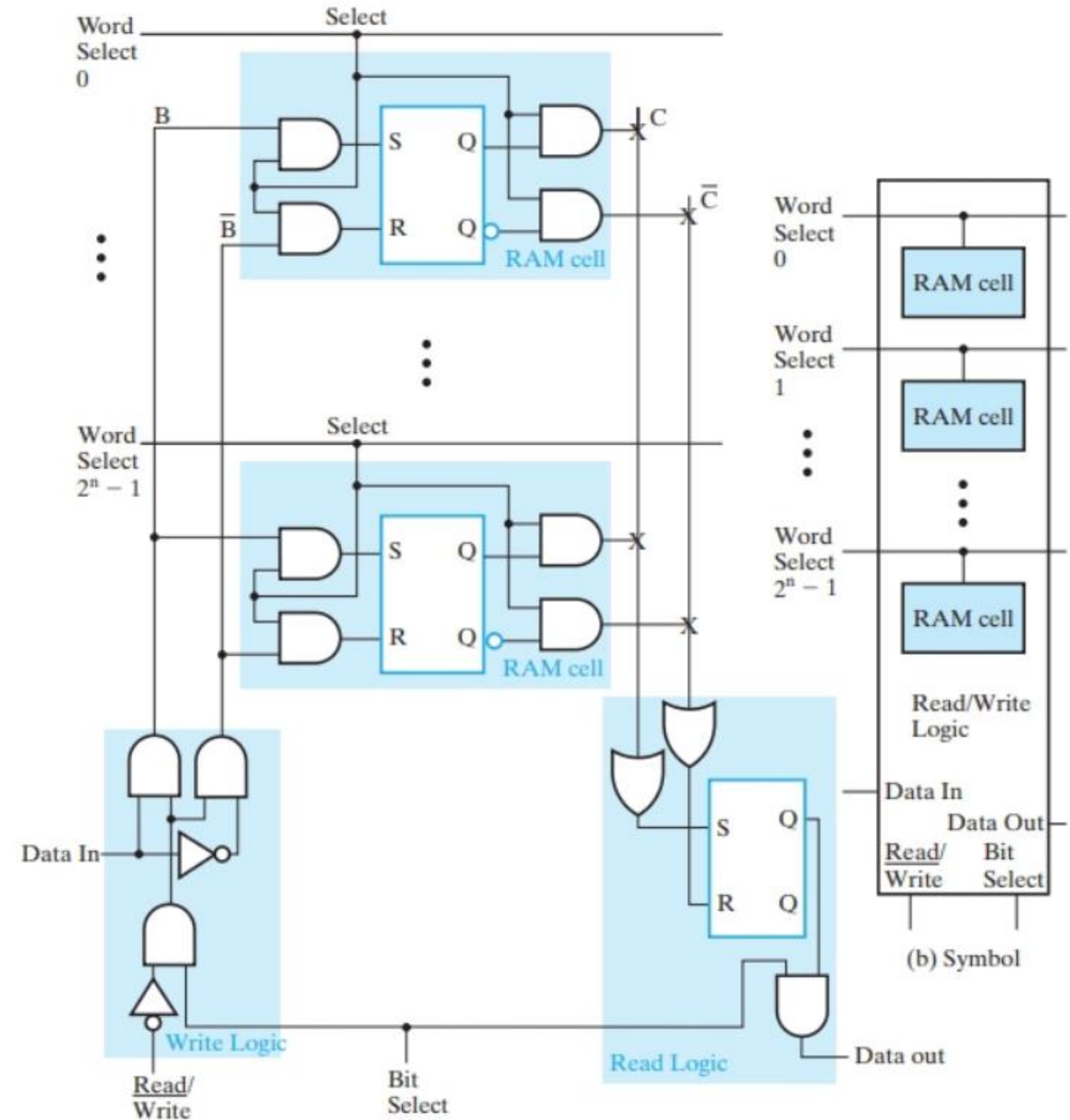
- If $Select = 1$, the stored content is determined by the values B, \bar{B}
- If $Select = 0$, both $C, \bar{C} = 0$
- $Select$ enables/disables the access to the cell
- RAM bit slice \rightarrow contains all of the circuitry associated with a single bit position of a set of RAM words



SRAM Bit Slice


- Every bit of our memory needs all this logic
- Can we design the circuit to be cheaper?
- In memory we can access only ONE location (=row) at a time
- We can decide to share the select, read, write logic of a single bit with all the bits of the same column!
- We call this component **BIT SLICE**

0	00101010
1	01011010
2	00001110
3	01010100
4	01110110
5	01100100
6	11001001
7	11101010

 

SRAM

- The loading of a cell latch is controlled by a signal **Word Select**
- You can require the access to the k bit of the word at the address 0 or 1 or 2 or ... $2^n - 1$*
- For «*Word Select 0*» = 0 The k bit of the word 0 remain unchanged
- For «*Word Select 0*» = 1 the stored content is determined by the values on B, \bar{B} that are determined in turn by the Write Logic
- This applies to one bit of the word
- Each RAM bit slice is interconnected with other to control all the bits of a word

 

16-Word by 1-Bit RAM Chip

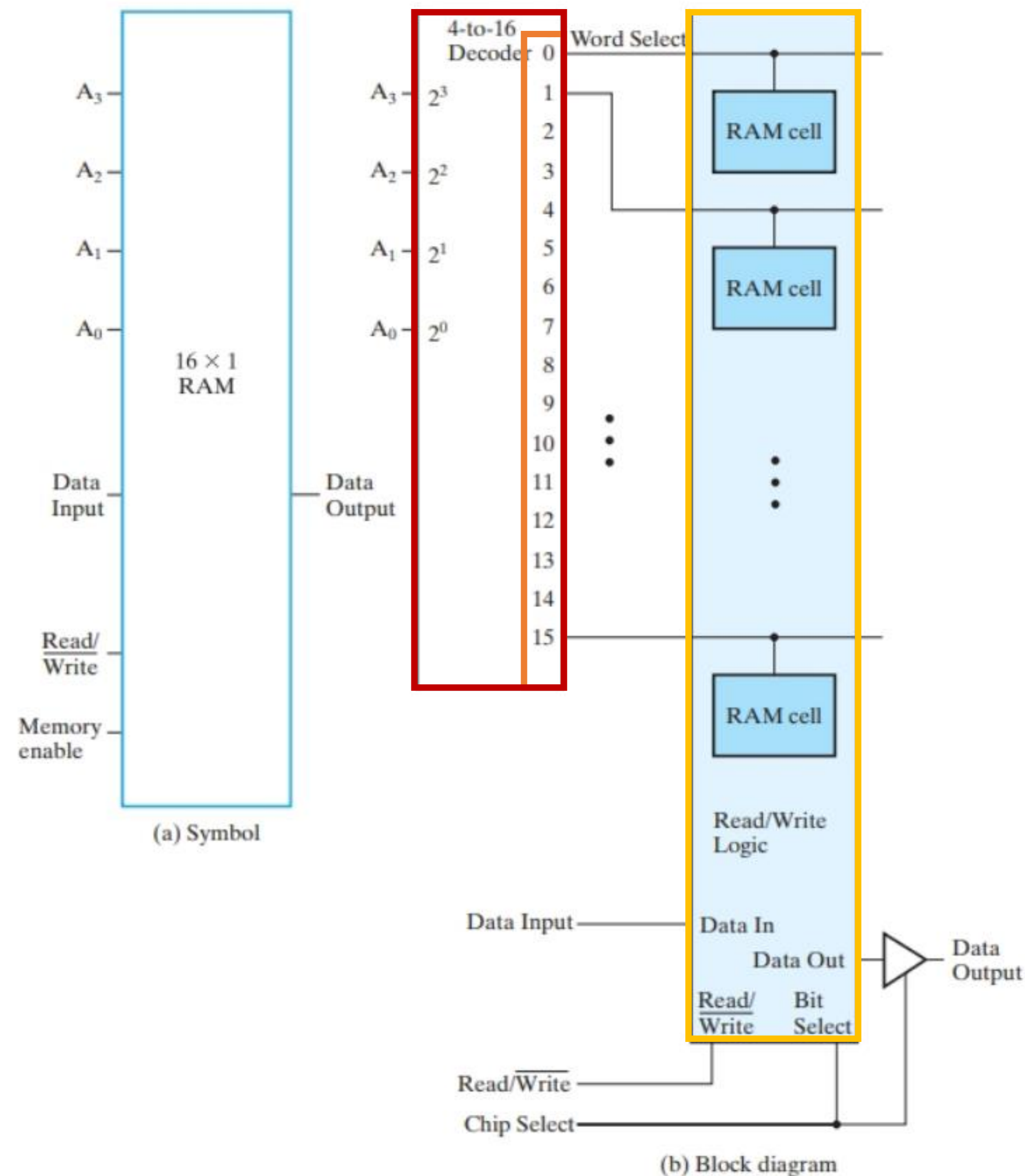


FIGURE 7-6
16-Word by 1-Bit RAM Chip

- For simplicity, we consider a SRAM chip with 16 one-bit words
- The internal structure of the RAM chip consists of a RAM bit slice having 16 RAM cells
- To select a word, we need 16 addresses
- To select 16 addresses, we need a 4-to-16 line decoder
- In this case, the address is composed of 4 bits ($16 = 2^4$)

A_3	A_2	A_1	A_0
-------	-------	-------	-------

16x1 SRAM chip with 4x4 RAM Array


 


FIGURE 7-7
Diagram of a 16 × 1 RAM Using a 4 × 4 RAM Cell Array

 - Different structure (to optimize space and components)
- 2D matrix of 16 RAM cells
- Selection through a 2-to-4-line row decoder to select the row and the column
- The address is composed of 4 bits



8x2 SRAM chip using 4x4 RAM Cells Array


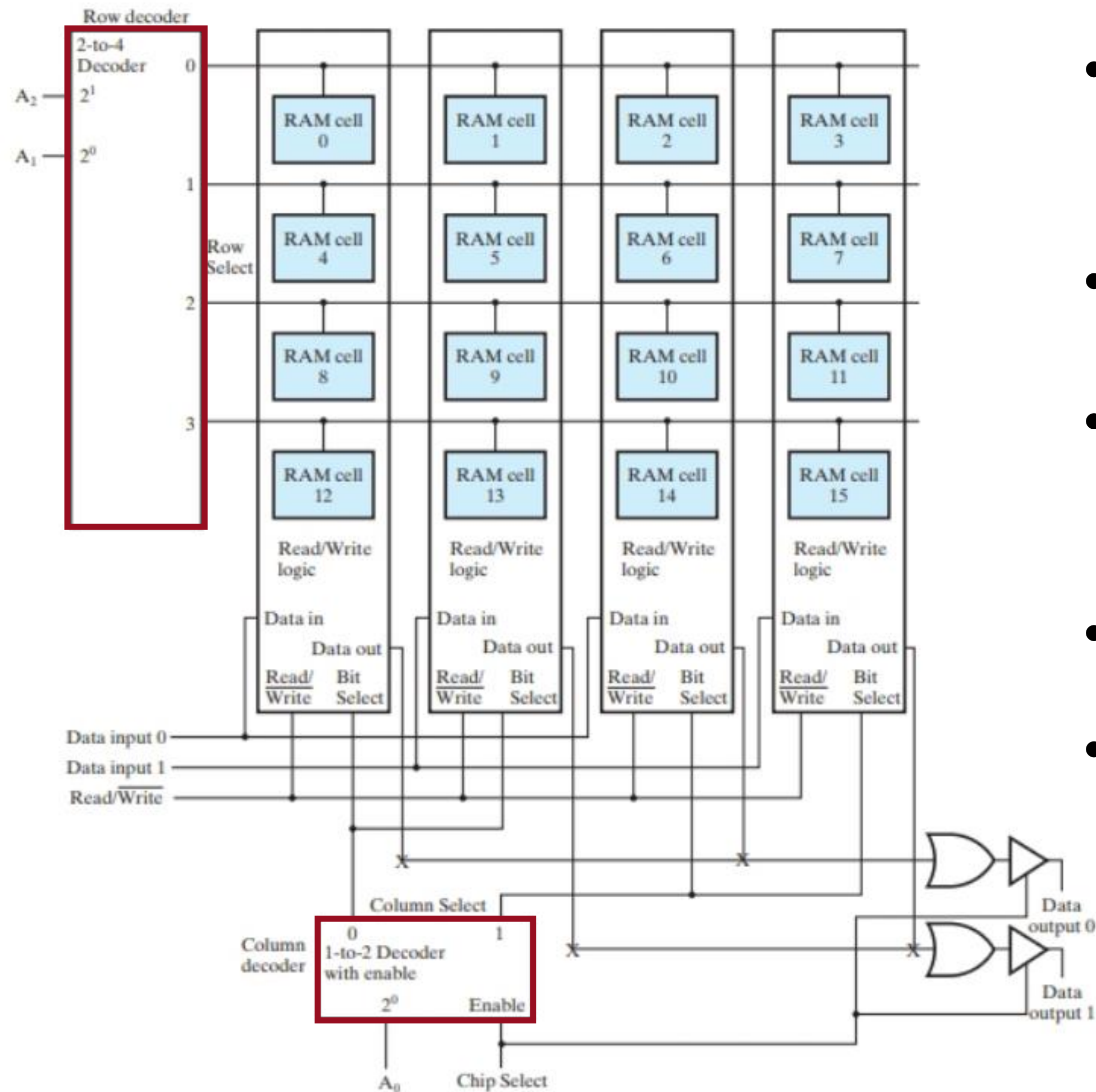


FIGURE 7-8
Block Diagram of an 8×2 RAM Using a 4×4 RAM Cell Array

 - Chip SRAM 8×2 (8 words of two bits each)
- Same approach of the previous example
- The number of bit in the address to identify a word: 3 ($8 = 2^3$)
- 2 bits in the address for the row decoder
- 1 bit in the address for the column decoder



8x2 SRAM chip using 4x4 RAM Cells Array

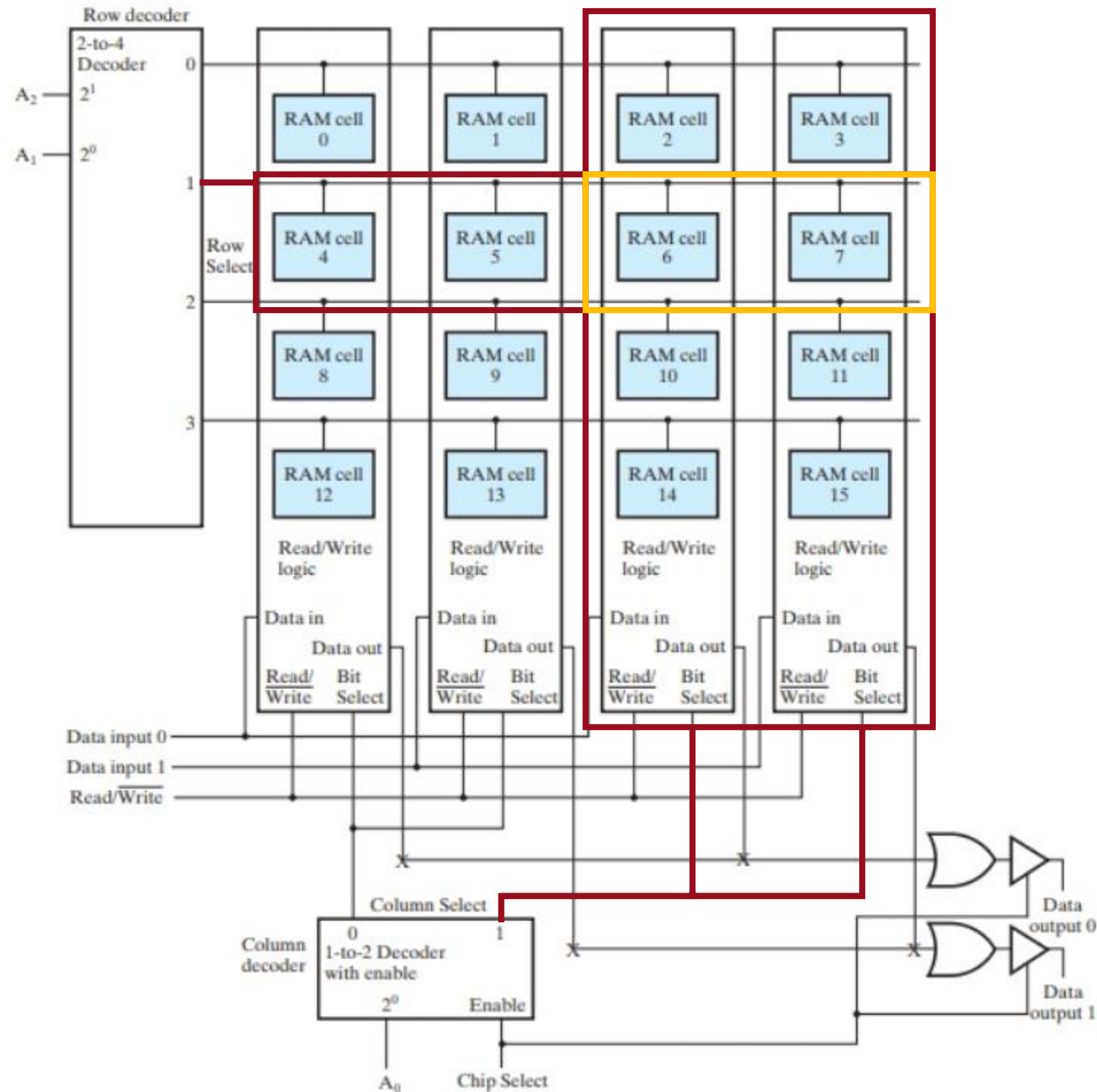


FIGURE 7-8
Block Diagram of an 8×2 RAM Using a 4×4 RAM Cell Array

Example: $A = 011_2$

A_2	A_1	A_0
0	1	1

- Row decoder:
 - Selected cells: 4, 5, 6, 7
- Column decoder:
 - Selected cells: 2, 6, 10, 14, 3, 7, 11, 15
- Selected word: cells 6 and 7 (2 bits)


Example SRAM chip

- We want to design a SRAM 32K x 8
 - Namely: with 32K words of 8 bits

([Cypress SRAM CT62256.pdf](#))



 - This SRAM chip contains a total of 256K bits (32K x 8)
- The minimum number of addresses from 32K words is k such that: $2^k \geq \text{words}$ is true
- $2^k \geq 32 \cdot 1024 \Rightarrow k \geq \log_2 32768 \Rightarrow k \geq 15$
- To make the number of rows and columns in the array equal:
 - $nrows\ ncolums = \sqrt{256K} = \sqrt{(256 \cdot 1024)} = 512 = 2^9$




since we address the words (groups of 8 bits) and not the individual bits, we just need $9-3=6$ bits


Recap

0	0	0	1	0	1	0	1	0
1	0	1	0	1	1	0	1	0
2	0	0	0	0	1	1	1	0
3	0	1	0	1	0	1	0	0
4	0	1	1	1	0	1	1	0
5	0	1	1	0	0	1	0	0
6	1	1	0	0	1	0	0	1
7	1	1	1	0	1	0	1	0


ONE BIT LOGIC

 

BIT COLUMN LOGIC (RAM slices)

 

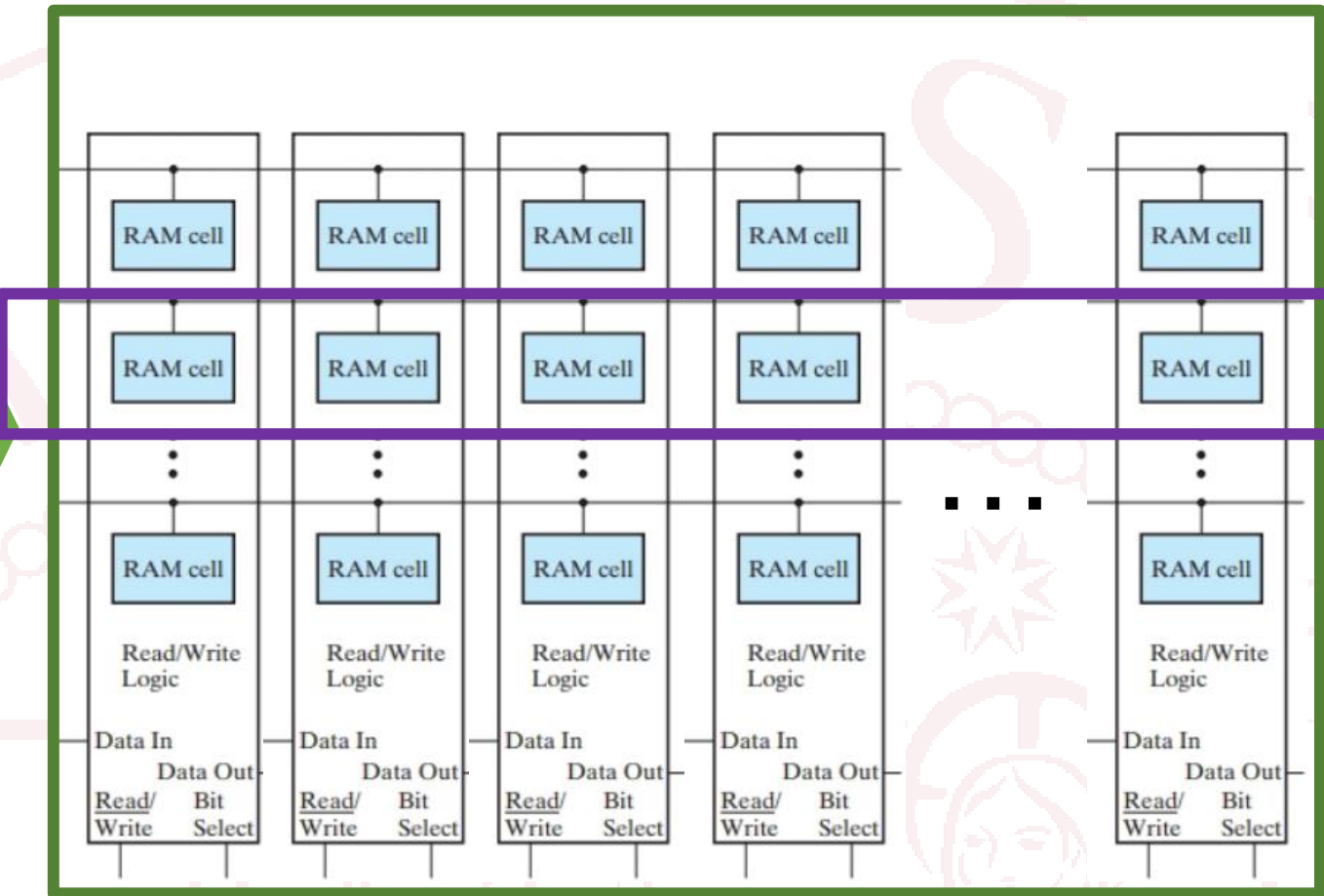LOTS OF RAM SLICES = ALL RAM (organized as an array)



The bits of a WORD (memory location) are stored on multiple RAM slices

DRAM: Dynamic Random Access Memory

- Low cost and high storage capacity
- Very common in the memory in our current computers
- Similar implementation to SRAM, but with **significant differences**:
 - The electronic design is considerably more challenging
 - The storage of information is inherently only temporary (dynamic in the name)
 - The information must be periodically refreshed

DRAM Cell

- From the electronic point of view, a DRAM consists of a transistor (T) and a capacitor (C)
- If sufficient charge is stored on the capacitor, the stored value is 1, otherwise is 0
- The transistor acts much like a switch:
 - When the switch is open, the charge in C remains fixed (the information is stored)
 - When the switch is closed, the charge can flow into and out of the C from the external Bit Line (B)
- These operations refer to the cell readings/writings

 


FIGURE 7-12
Dynamic RAM cell, hydraulic analogy of cell operation, and cell model

DRAM Cell: hydraulic analogy

- With closed valve (T opened):

- $C = 1$
- $C = 0$

storage

- With opened valve (T closed):

- $B = 0 \rightarrow 1; C = 0 \rightarrow 1$
- $B = 1 \rightarrow 0; C = 1 \rightarrow 0$

write

- With opened valve (T closed):

- $C = 1; B = +dC = 1$
- $C = 0; B = -dC = 0$

read

 



FIGURE 7-12

Dynamic RAM cell, hydraulic analogy of cell operation, and cell model

- In the read operation, the content in C is destroyed (**destructive read**)
- To be able to read the original value in the future, a **restore operation** is needed
- Also with the closed valve (T opened), there are some leaks of charge → **refresh**

DRAM bit slice

- *Latch D as model for a DRAM cell*

 

- From the standpoint of cost per bit, the two RAM bit slices are different:
 - DRAM \rightarrow Transistor + capacitor (2)
 - SRAM \rightarrow 6 transistors (6)
- From the cell structure, the two RAM bit slices are logically similar, but the number of components is definitely lower.
- Given a fixed size, the number of cells in SRAM $<$ number of cells in DRAM
- DRAM capacity is higher \rightarrow used in large memories


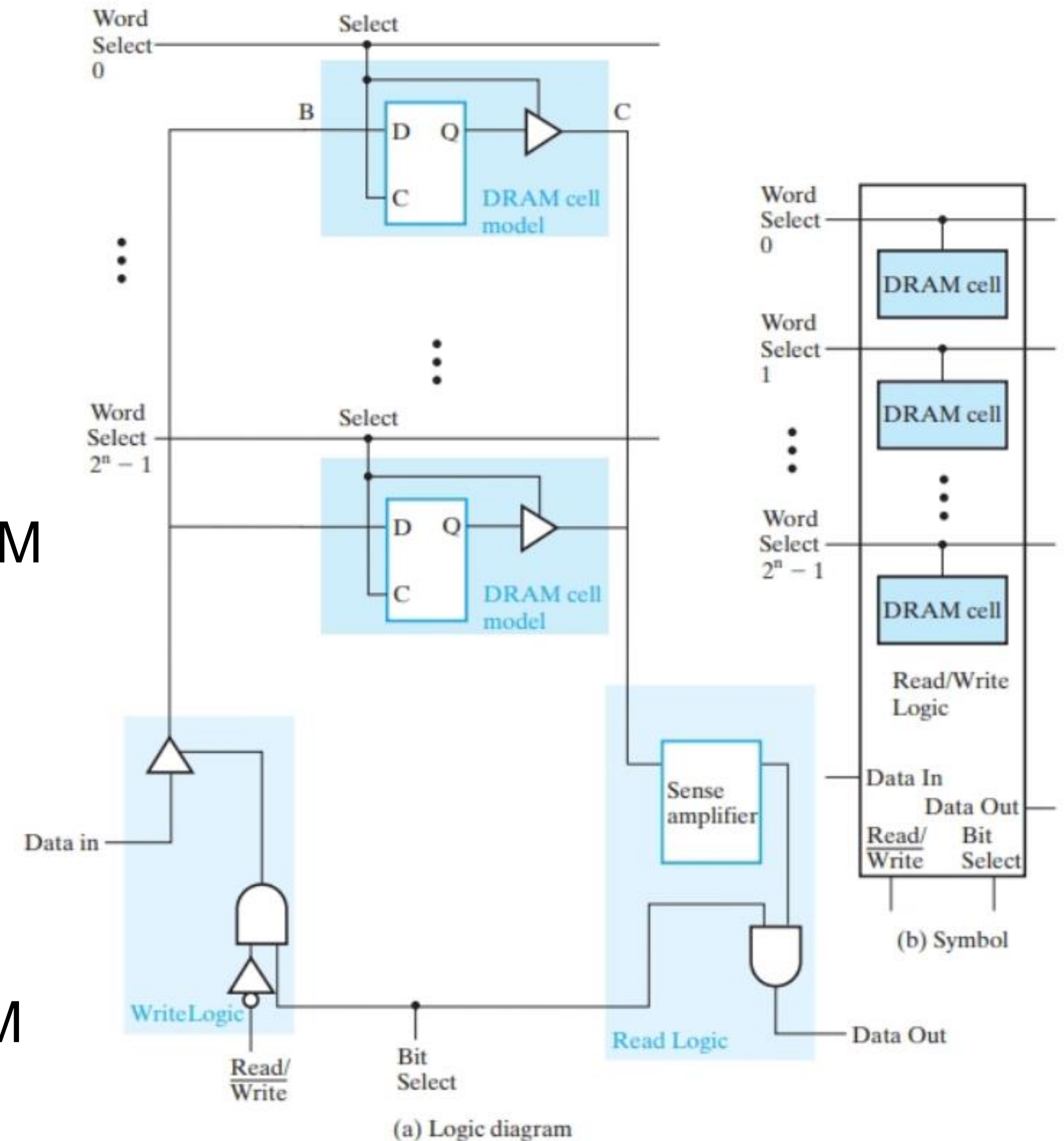


FIGURE 7-13
DRAM Bit-Slice Model

Addressing in DRAM memories

- Large DRAM requires 20 or more address bits (e.g., 20 address pins in each DRAM chip)
- To reduce the number of pins, the structure is slightly different than SRAM
- The DRAM address is applied serially in two parts:
 - The **row address** first
 - The **column address** second
- The row and column addresses are stored in registers.


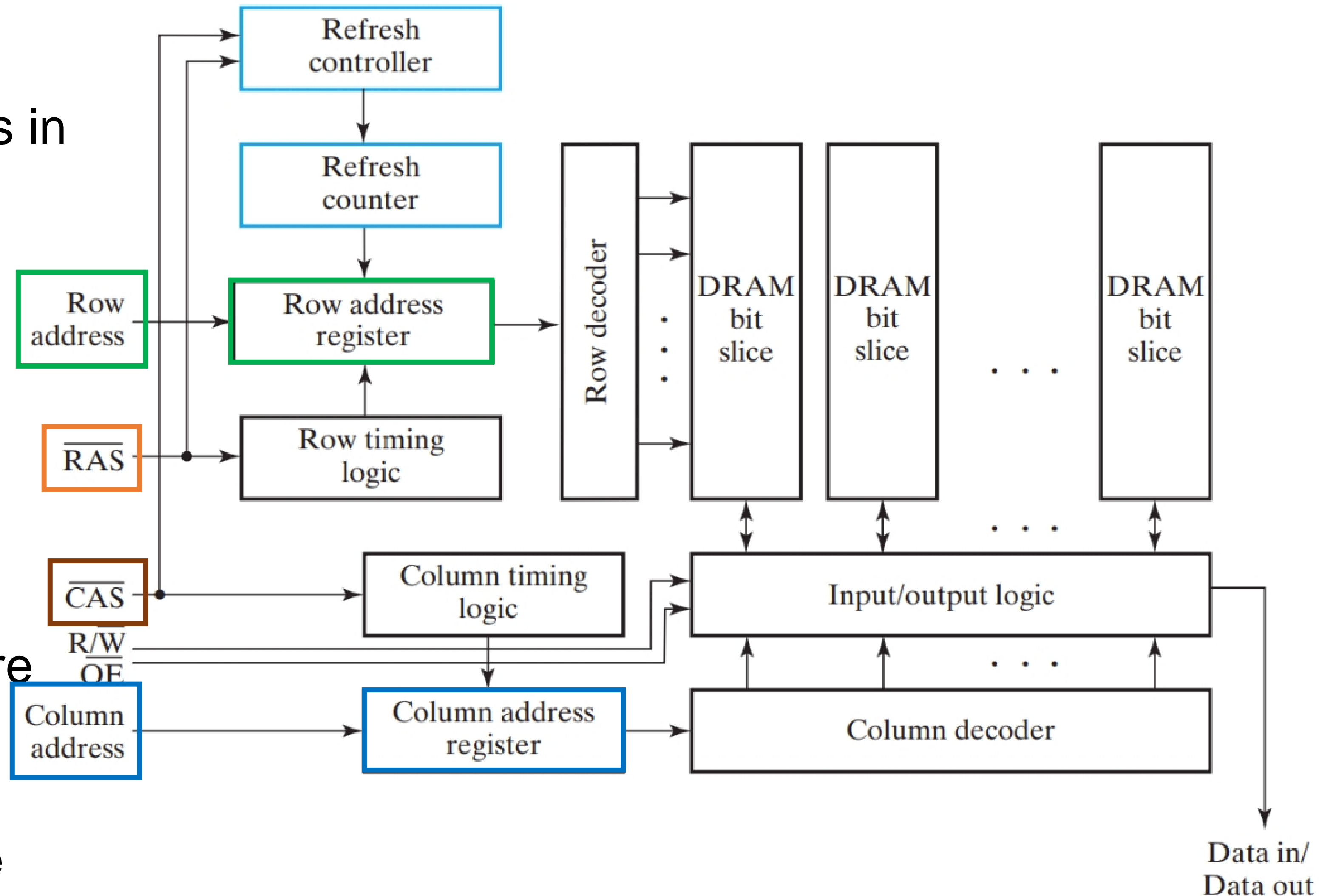
RAS (Row Address Strobe) and ***CAS*** (Column Address Strobe) are exploited to enable the time access to registers



□ **FIGURE 7-14**
Block Diagram of a DRAM Including Refresh Logic

Timing for DRAM memories: Write

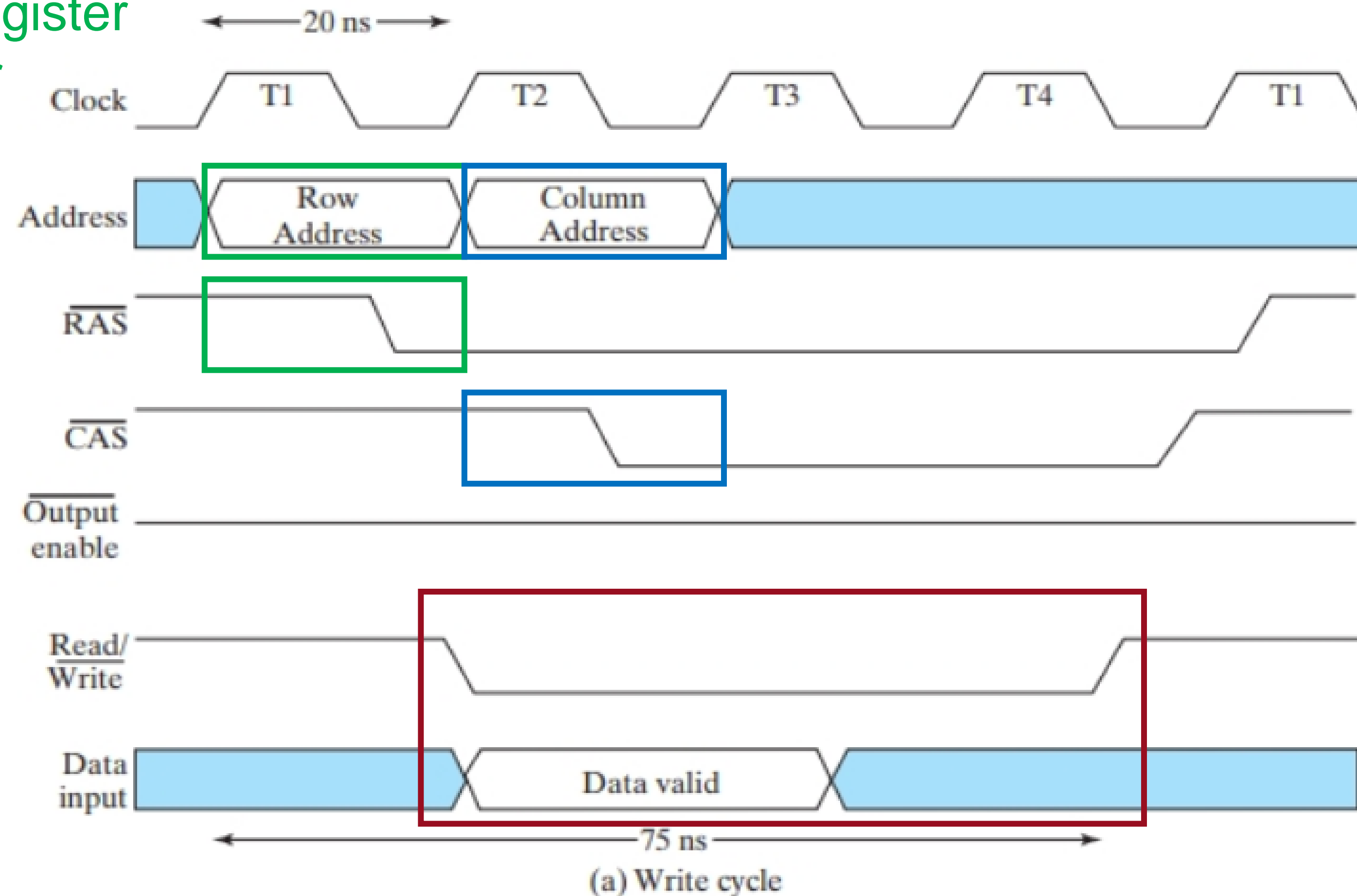
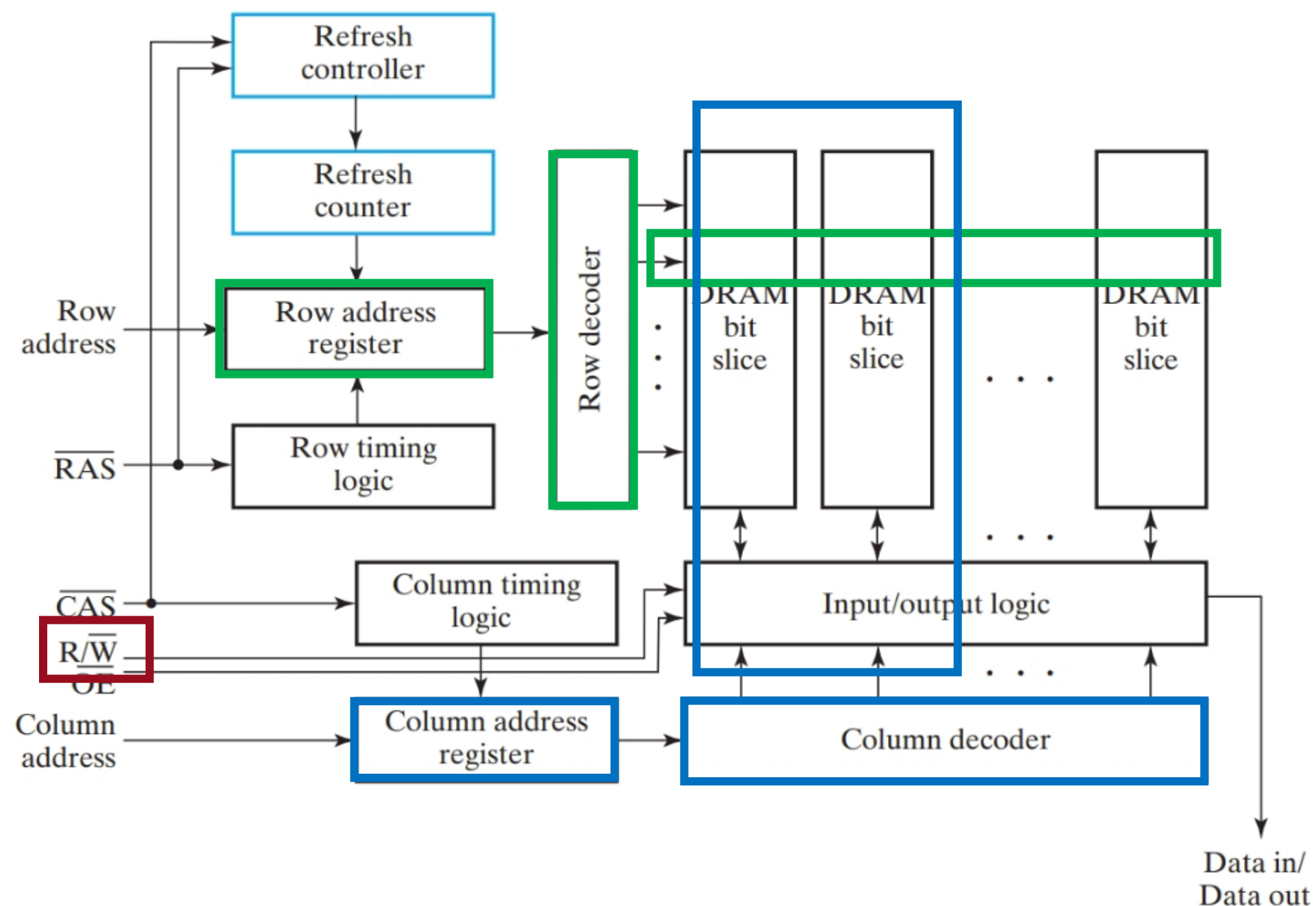
1. Row address is applied to the address input
2. $\text{RAS} \rightarrow 0$, row address is loaded into the register
3. Row address is applied to the row decoder
4. Row is selected
5. Column address
6. $\text{CAS} \rightarrow 0$, column address is loaded
7. Column address is applied to the column decoder
8. Column is selected



- $\text{RW} \rightarrow 0$, Input data are written in the selected cells
- The stored data in all of the other cells are **restored**

Timing for DRAM memories: read

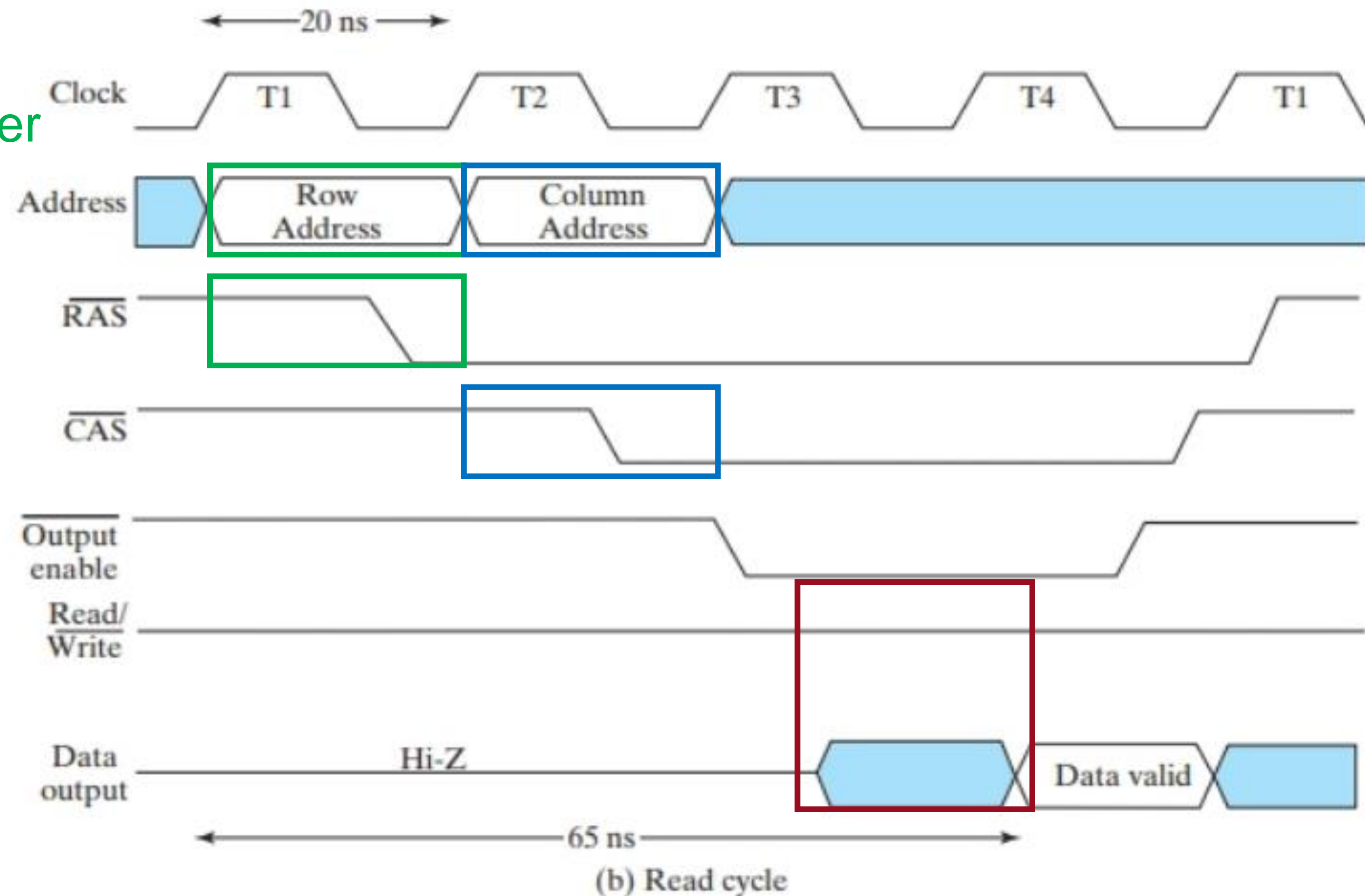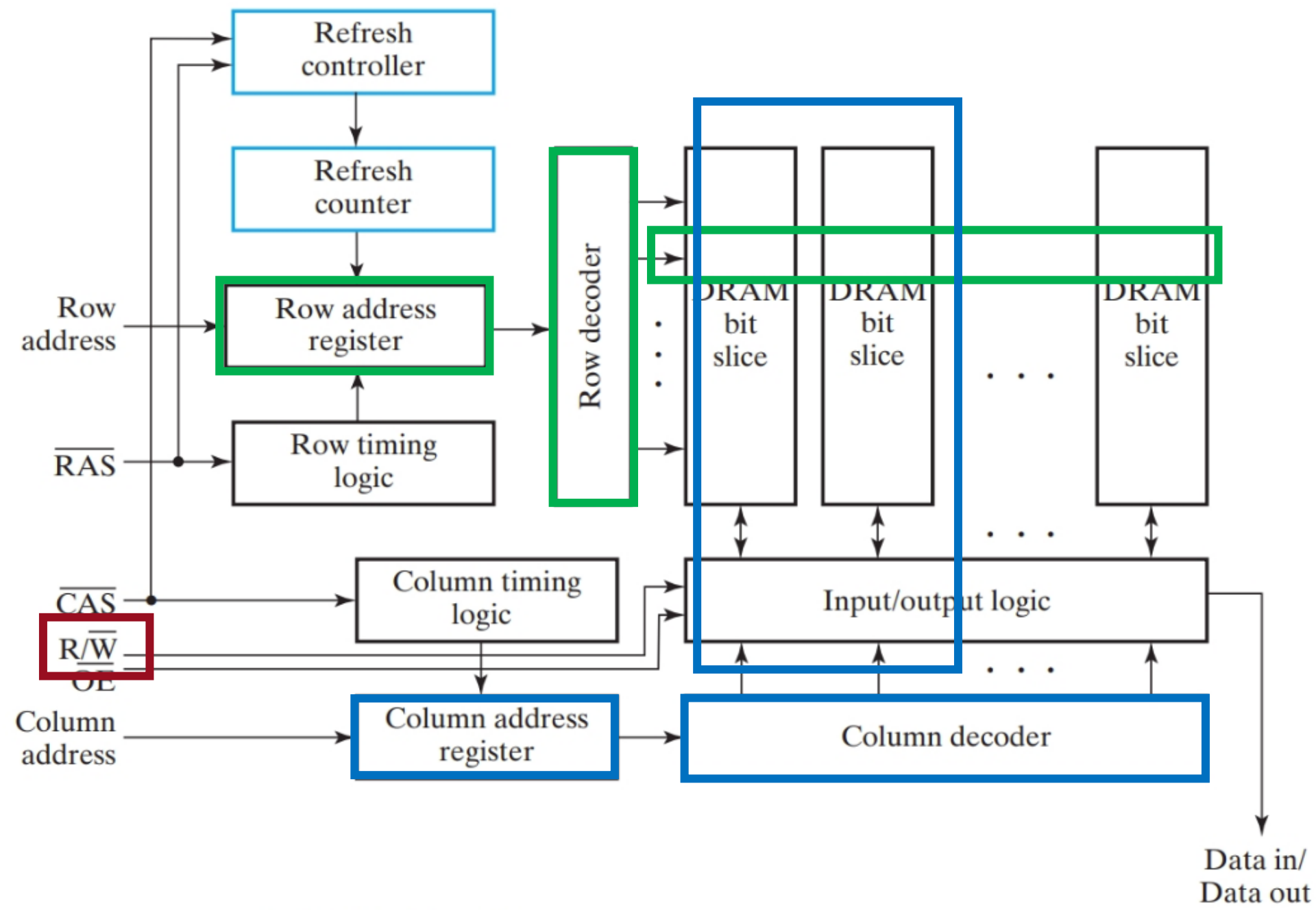
1. Row address is applied to the address input
RAS $\rightarrow 0$, row address is loaded into the register
2. Row address is applied to the row decoder
3. Row is selected
4. Column address
5. CAS $\rightarrow 0$, column address is loaded
6. Column address is applied to the column decoder
7. Column is selected



- RW $\rightarrow 1$, The selected cells are read
- The stored data in all of the other cells are **restored**

Refresh in DRAM memories

- **Refresh counter:** the address of the row of DRAM cells to be refreshed
- **Refresh controller:** enables the refresh
- Three ways to trigger a refresh:
 1. **RAS-only refresh**
 - Refresh of a specific row
 - It must be applied from outside
 2. **CAS-before-RAS refresh**
 - $\text{CAS} \rightarrow 0$ and $\text{RAS} \rightarrow 0$
 - It is controlled by the refresh counter
 3. **Hidden refresh**
 - Following a normal read or write
 - The time taken to read/write data is significant

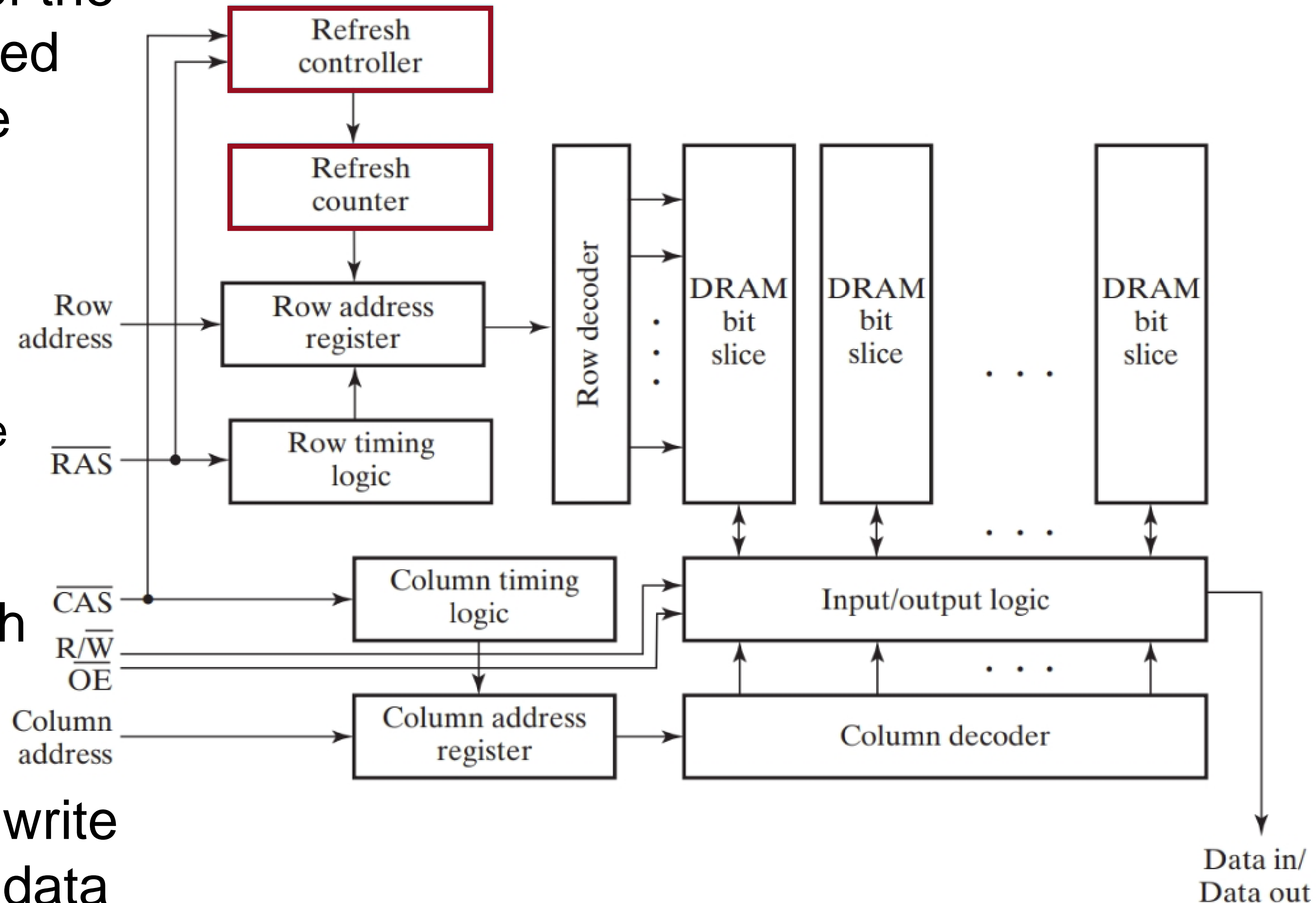


□ **FIGURE 7-14**

Block Diagram of a DRAM Including Refresh Logic


Refresh in DRAM memories

- Each row of a DRAM chip requires refreshing within a specified maximum refresh time, typically ranging from 16 to 64 ms.
- Distributed Refresh:** refreshes may be performed at evenly spaced points in the refresh time
 - Example:** 4M x 4 DRAM has a refresh time of 64 ms
 - $N_r = 4 \cdot 1024 = 4096$ rows to be refreshed
 - A single refresh** is executed in $t_r = 60 \text{ ns}$
 - The refresh interval for distributed refresh** is: $t_i = \frac{64 \text{ ms}}{4096} = 15.6 \mu\text{s}$
 - A total time out for refresh is $T_R = t_r \cdot N_R = 60 \text{ ns} \cdot 4096 = 0.00024576 \approx 0.25 \text{ ms}$
 - During any refresh cycle, no DRAM reads or writes can occur

 

Refresh in DRAM memories

- Each row of a DRAM chip requires refreshing within a specified maximum refresh time, typically ranging from 16 to 64 ms.
- Burst refresh:** all the refreshes may be performed one after the other (**refresh time**)
 - Example:** 4M x 4 DRAM with refresh time of 64 ms
 - $N_r = 4 \cdot 1024 = 4096$ rows to be refreshed
 - A **single refresh** is executed in $t_r = 60 \text{ ns}$
 - The **4096 refreshes** are performed one after the other
 - A total time out for refresh is $T_R = t_r \cdot N_R = 60 \text{ ns} \cdot 4096 = 0.00024576 \cong 0.25 \text{ ms}$
 - The memory is busy for the next 0.25 ms

 

Synchronous DRAM (SDRAM)

Basic concepts:

- In the modern computer, the CPU **does not** directly interact with DRAM
- There is a memory hierarchy: CPU \leftrightarrow Cache (L1, L2) \leftrightarrow Memory
- The reads are in the form of a **line (bytes in contiguous addresses in memory)**
- For effectiveness, it is preferable to **read out of all the bits in a row for each read operation**

16 MB SDRAM

- Similar to the structure of a DRAM
- The addition of a **clock** for synchronous operation
- Control logic is much more complex

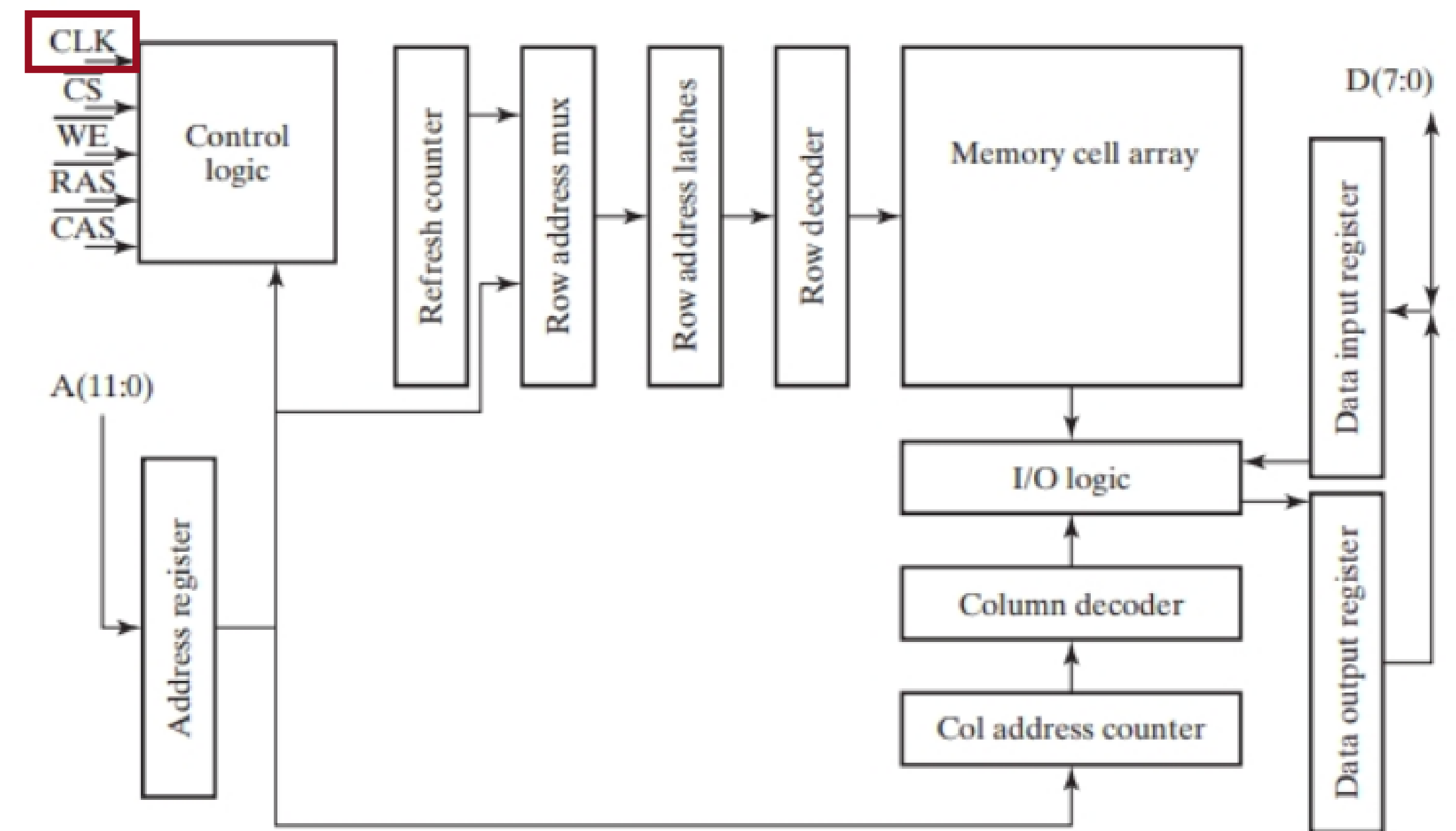


FIGURE 7-16
Block Diagram of a 16 MB SDRAM

Synchronous DRAM (SDRAM)

Esempio 16 MB SDRAM:

- $N_{bits} = 16 \cdot 2^{20} \cdot 8 = 134217728 \text{ bits}$
- $N_{rows} = 8192, N_{cols} = 16384 \Rightarrow N_{rows} \cdot N_{cols} = N_{bits}$
- $N_{ARbit} = \log_2 8192 = 13 \text{ bits}$
- $N_{ACbit} = \log_2 \frac{16384}{8 \text{ bit}} = 11 \text{ bits}$
- $N_{ARbit} + N_{ACbit} = 24 = \log_2(16 \cdot 2^{20})$
- **Row address** is applied
- The whole row is loaded into the **I/O logic**
- **Column address** is applied
- Data in the **output register**, 1 bit per clock


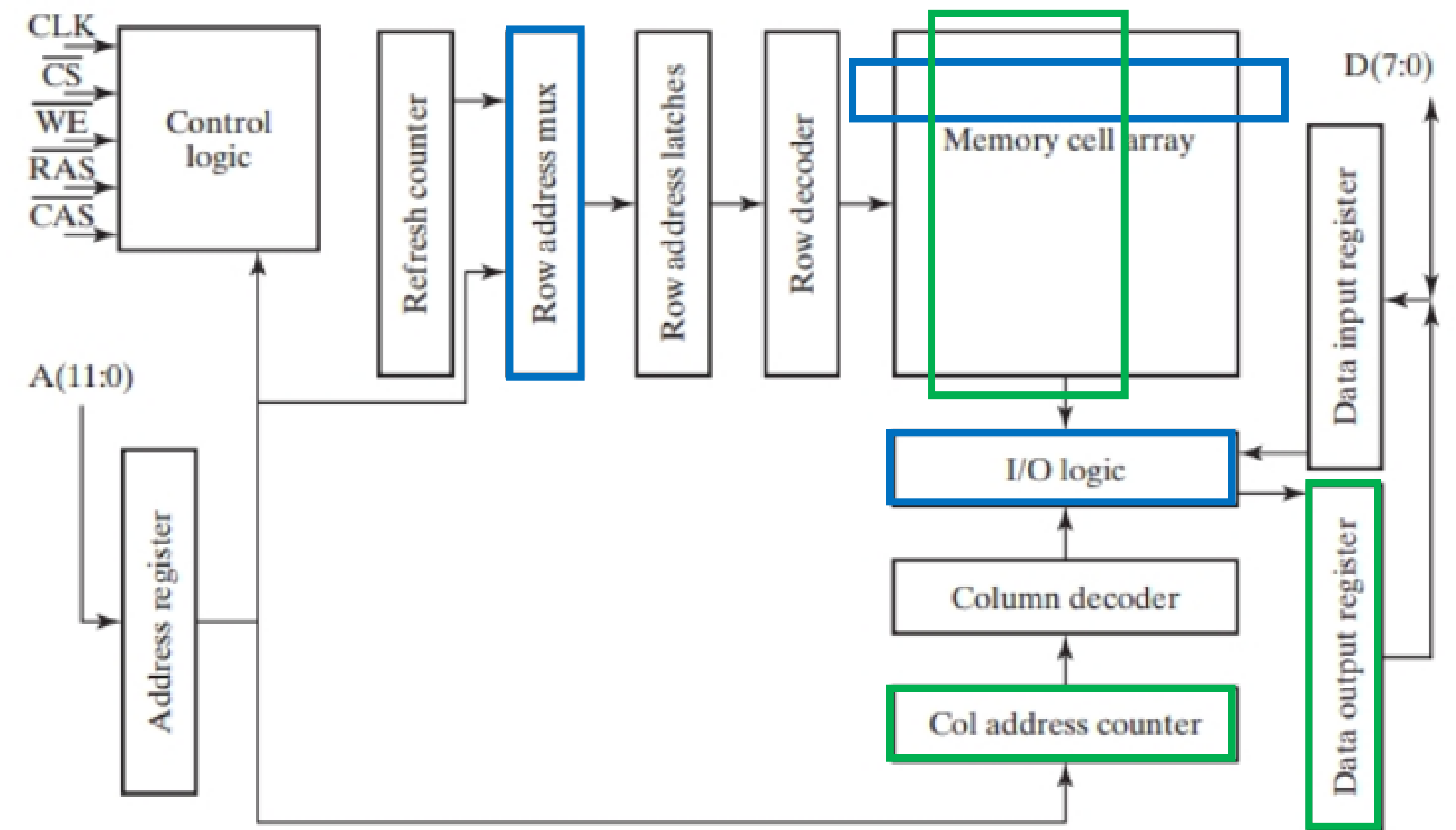


FIGURE 7-16
Block Diagram of a 16 MB SDRAM

Synchronous DRAM (SDRAM)

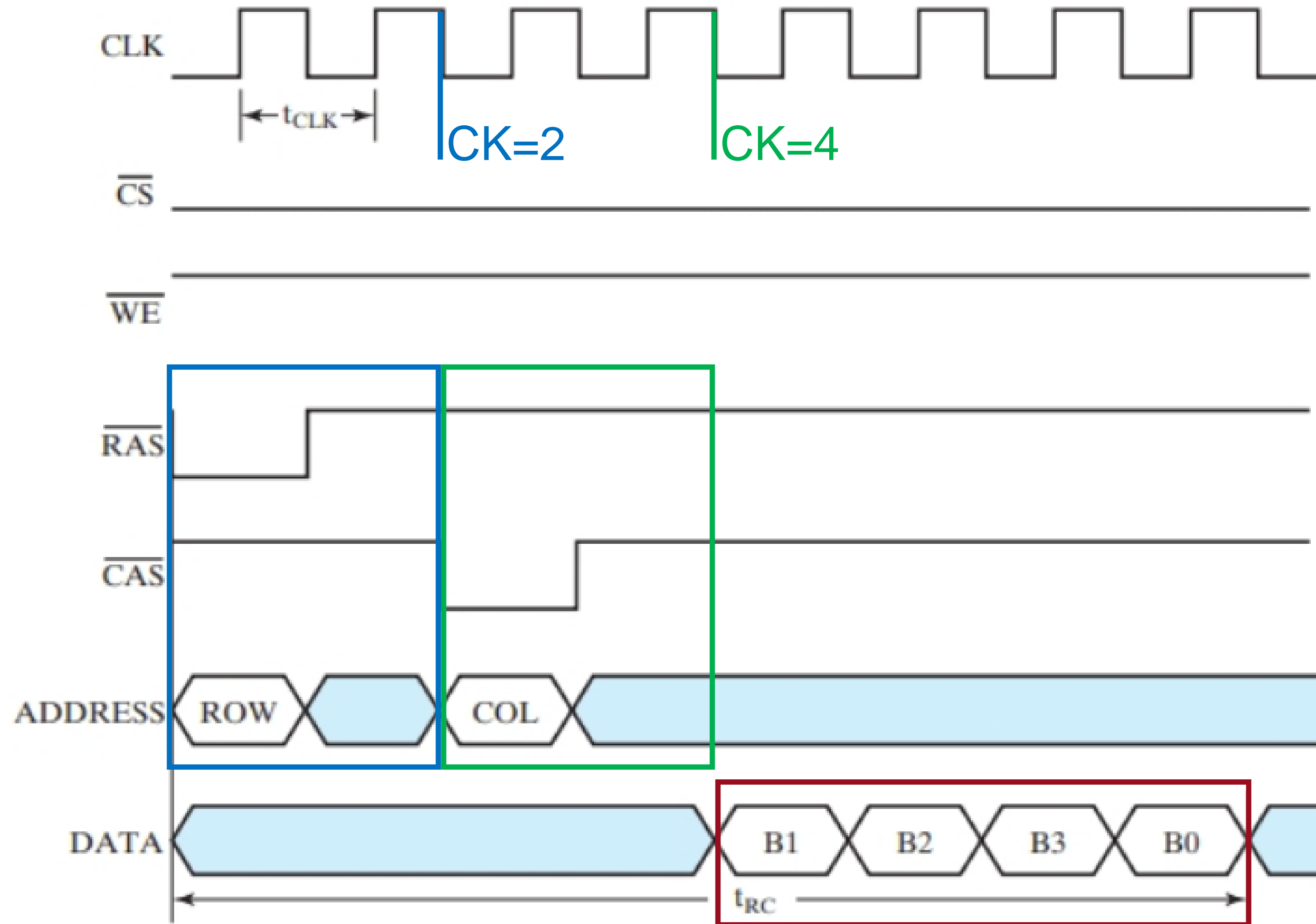

□ **FIGURE 7-17**
Timing Diagram for an SDRAM

- **Row address** into the register
- **Reading of the row**
- **Column address** into the register
- **Reading of the bytes**
- **Output of 4 bytes**, one per clock cycle

SDRAM vs. DRAM

DRAM

- Read cycle time: $t_{RC} = 60 \text{ ns}$
- 1 byte per read cycle time
- $\text{BitRate} = \frac{1}{t_{rc}} = 16.67 \text{ MB/s}$

SDRAM

To read 4 bytes:

- Clock: $t_{CLK} = 7.5 \text{ ns}$
- $t_{RC} = 7.5 \text{ ns} \cdot (4 \text{ fixed clock cycles} + 4 \text{ clock cycles}) = 60 \text{ ns}$
- $\text{BitRate} = \frac{1}{t_{rc}} = 66.67 \text{ MB/s}$

To read 8 bytes:

- $t_{RC} = 7.5 \text{ ns} \cdot (4 \text{ fixed clock cycles} + 8 \text{ clock cycles}) = 90 \text{ ns}$
- $\text{BitRate} = \frac{8}{t_{RC}} = 88.89 \text{ MB/s}$

To read the entire row (2048 bytes):


- $t_{RC} = 7.5 \text{ ns} \cdot (4 \text{ fixed clock cycles} + 2048 \text{ clock cycles}) = 15390 \text{ ns}$
- $\text{BitRate} = \frac{2048}{t_{RC}} = 133.07 \text{ MB/s}$

**It approximates a byte
per clock cycle** ←

Disclaimer

Figures from *Logic and Computer Design Fundamentals*,
Fifth Edition, GE Mano | Kime | Martin

© 2016 Pearson Education, Ltd

 

Questions

