

# Computer Design Basics – Part A

Instruction cycle, the Control Word

**Gloria Beraldo** (gloria.beraldo@unipd.it)


Department of Information Engineering, University of Padova

## Topics:

- Control and microoperations
- Instruction Set Architecture
- Single-cycle computer

## Book Reference:

- Chapter 8

 

# Datapath representation and the Control Word

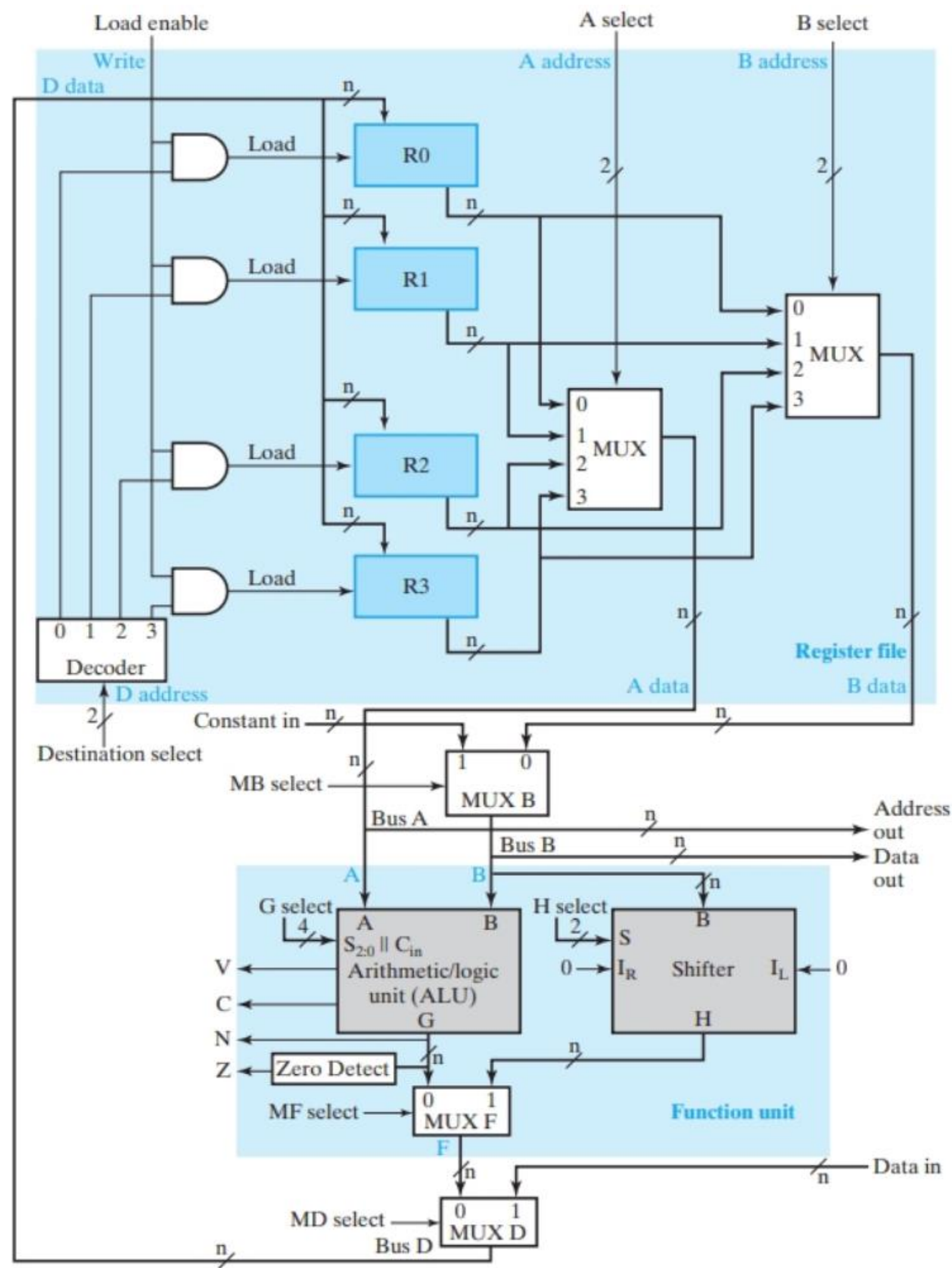


FIGURE 8-1  
Block Diagram of a Generic Datapath

- A typical datapath has more than four registers. A set of registers may be organized into a *register file*
- The size of the register file is  $2^m \times n$ , where  $m$  is the number of register address bits and  $n$  is the number of bits per register
- The select of the input, operations, output is executed via the **control word** that identifies them uniquely
- The operations are executed in a single clock cycle

$$2^2 = 4 \text{ registers}$$

# Datapaths: The Control Word (1)

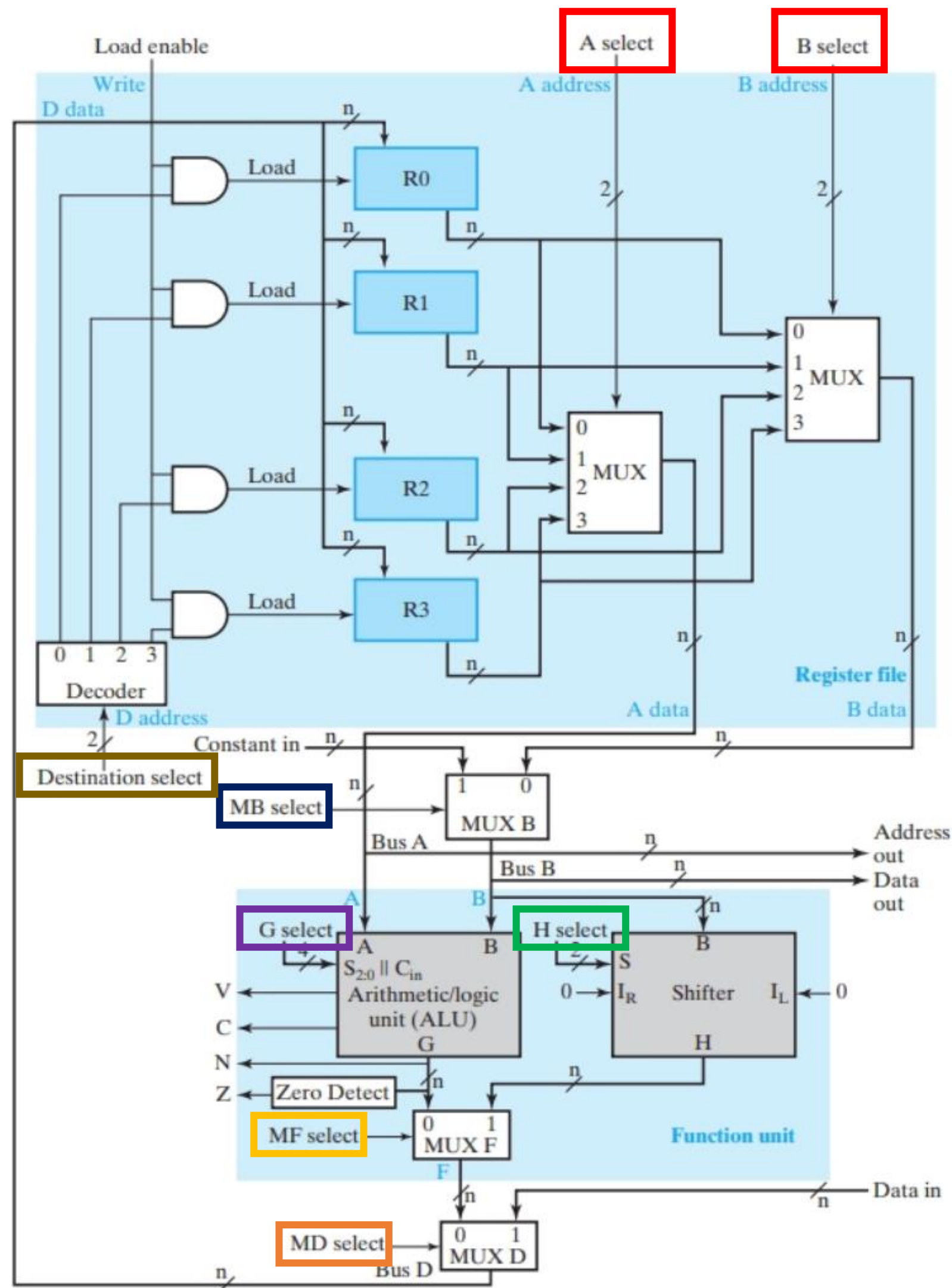


FIGURE 8-1  
Block Diagram of a Generic Datapath

- **A select, B select** → select which registers to use
- **G select** → selects the operations that the ALU has to execute
- **H select** → either passes the operand on Bus B directly through to the shifter output or selects a shift microoperation
- **MB select** → selects whether B is achieved by a constant from outside
- **MF select** → selects whether the output is achieved by the ALU or by the shifter
- **MD select** → selects the output of the function unit or an external data
- **D select** → selects the register where to write the result of the operation

$$2^2 = 4 \text{ registers}$$



# Datapaths: The Control Word (2)


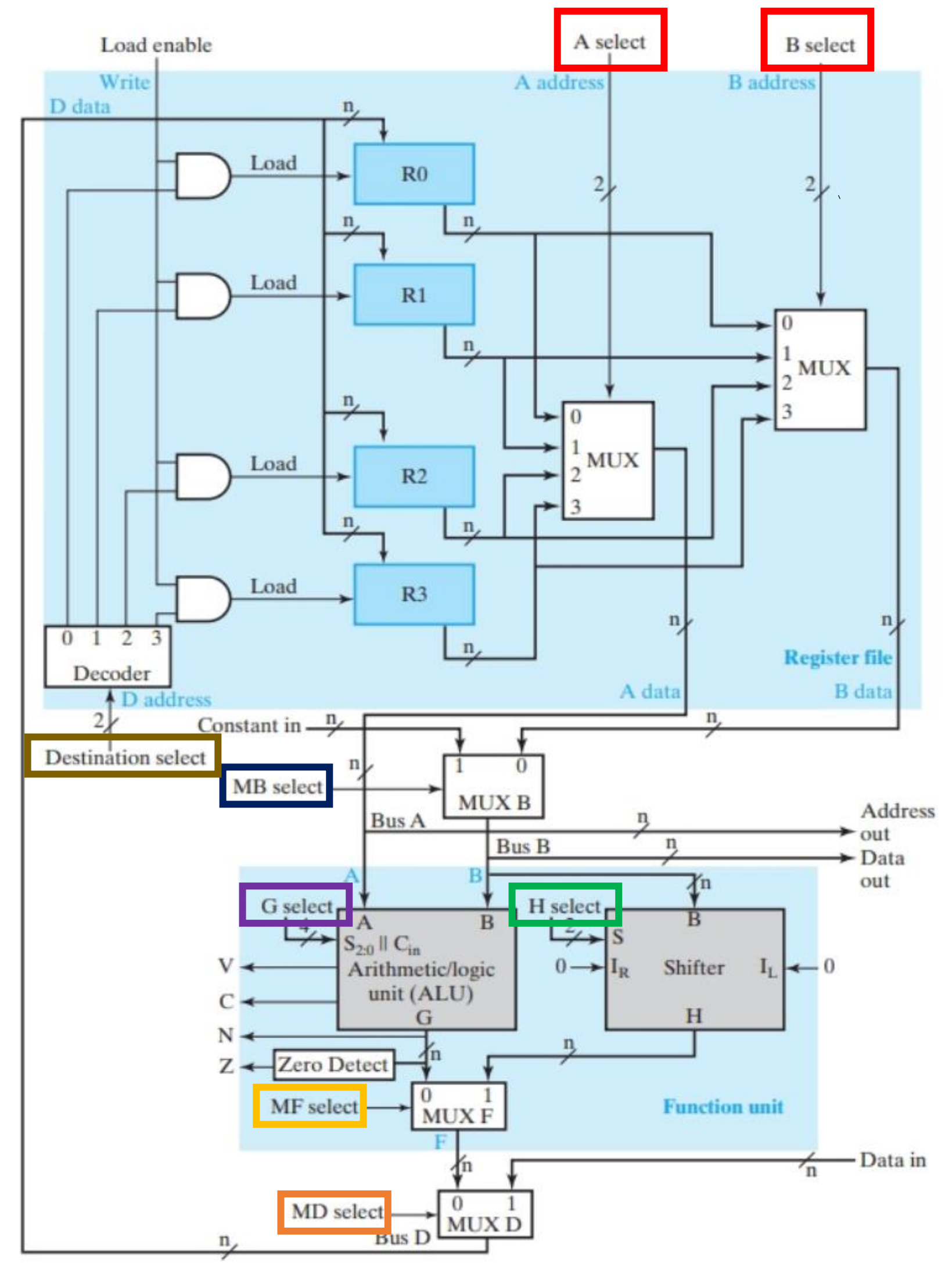
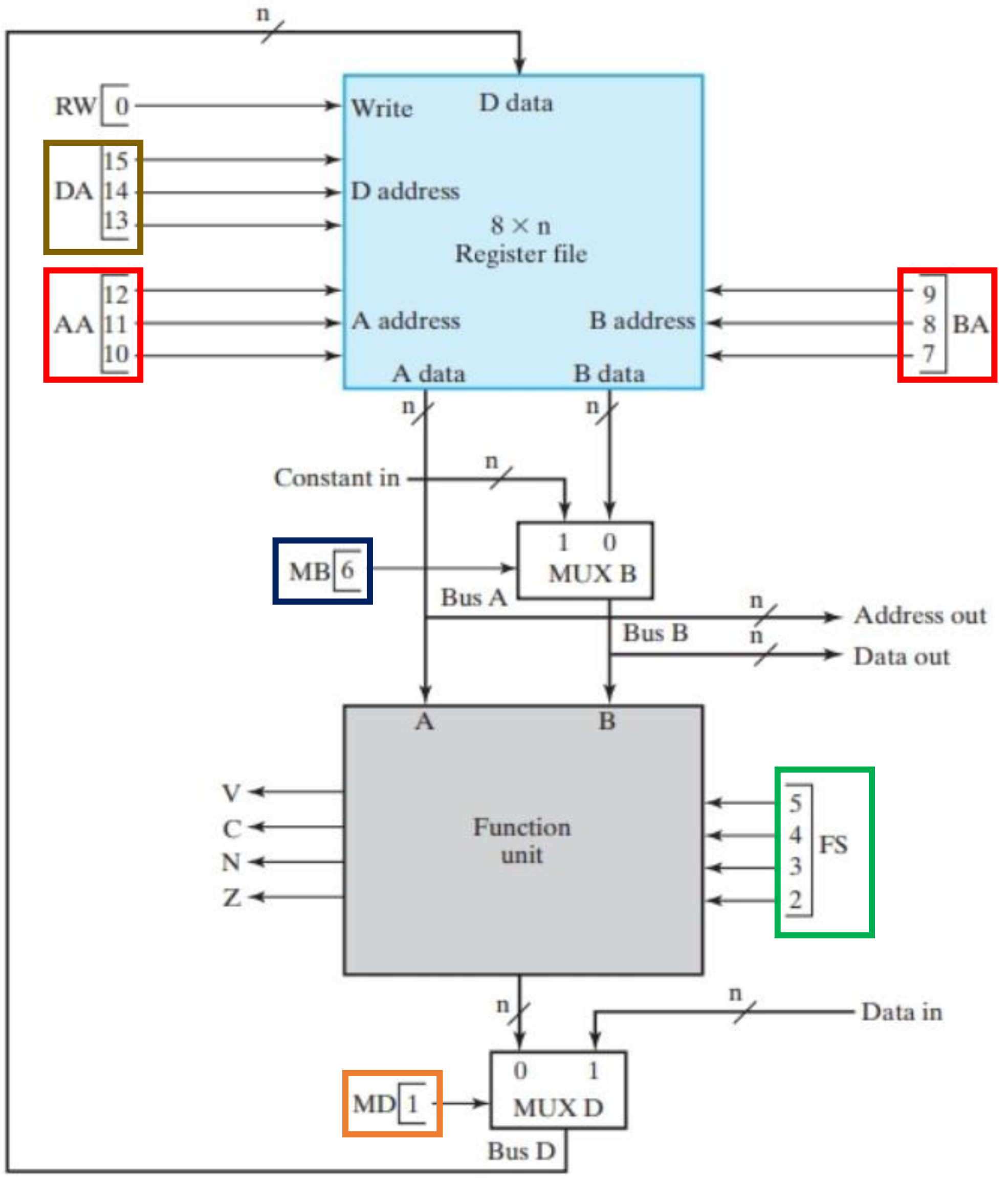


FIGURE 8-1 Block Diagram of a Generic Datapath

$2^2 = 4$  registers

 


(a) Block diagram

Now let's suppose to have  $2^3 = 8$  registers
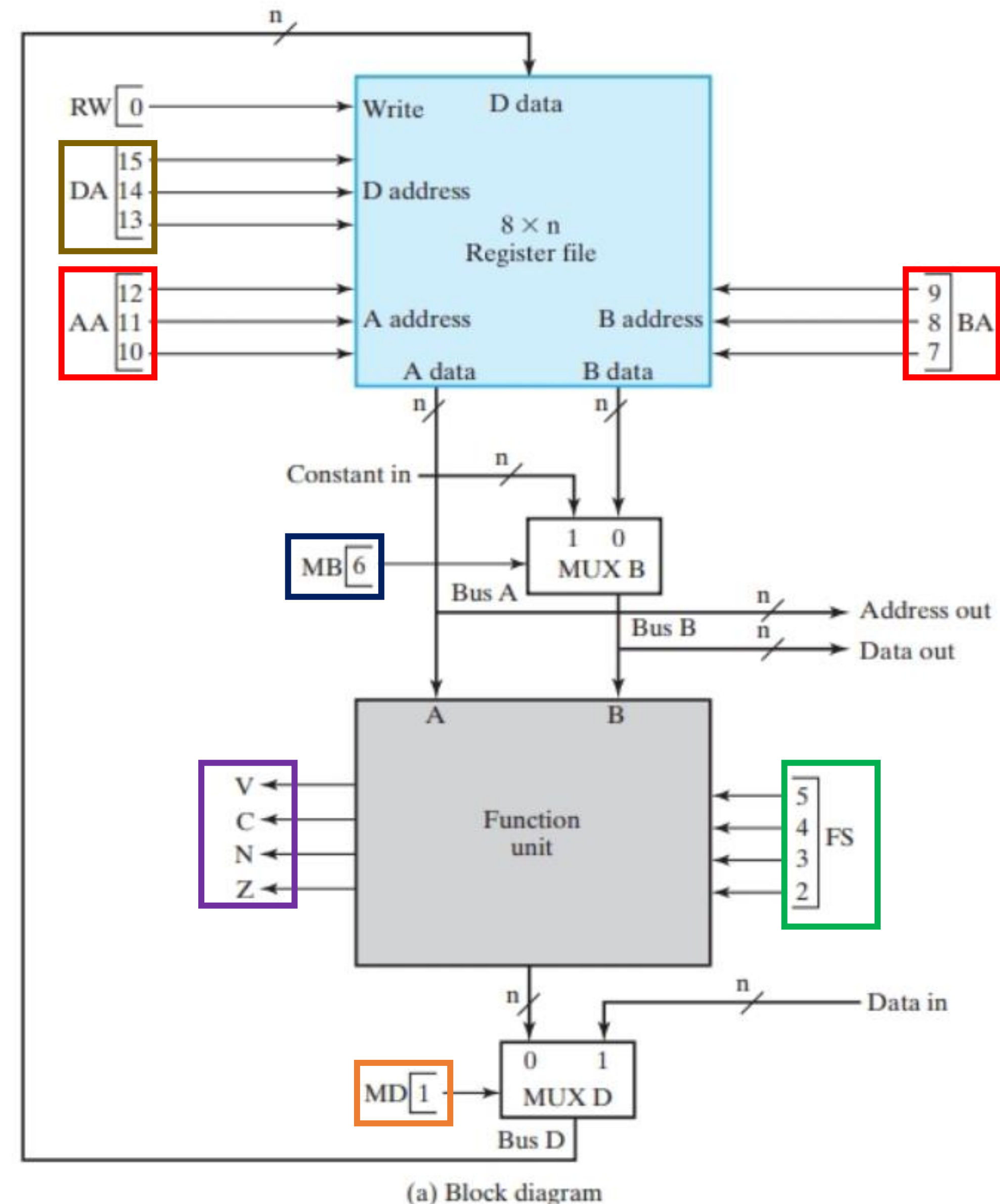
# Datapaths: The Control Word (3)

- **DA** identifies the address of the output register
- **AA** identifies the address of the register for the input A
- **BA** identifies the address of the register for the input B
- **MB** selects either the register selected by the BA field or a constant
- **FS** identifies the operation to execute (ALU or shifter)
- **MD** identifies the output
- **RW** identifies whether to write the output to the output register
- **Status bits**: V (overflow), C (carry), N (negative), Z (zero)




Now let's suppose to have  $2^3 = 8$  registers


 
# Datapaths: The Control Word (4)

- **DA** identifies the address of the destination register
- **AA** identifies the address of the register for the input A
- **BA** identifies the address of the register for the input B
- **MB** selects either the register selected by the BA or a constant from outside
- **FS** identifies the operation to be executed (ALU or shifter)
- **MD** identifies the output
- **RW** identifies whether to write the output to the destination register



(b) Control word

## Control word:


- 16-bit binary control input
- 7 fields
- Identify a microoperation uniquely



Now let's suppose to have  
 $2^3 = 8$  registers
 
# Datapaths: The Control Word (4)

- **DA** identifies the address of the destination register
- **AA** identifies the address of the register for the input A
- **BA** identifies the address of the register for the input B
- **MB** selects either the register selected by the BA or a constant from outside
- **FS** identifies the operation to be executed (ALU or shifter)
- **MD** identifies the output
- **RW** identifies whether to write the output to the destination register



(b) Control word

## Control word:

- 16-bit binary control input
- 7 fields
- Identify a microoperation uniquely



Now let's suppose to have  
 $2^3 = 8$  registers



# ALU: Arithmetic/Logic Unit

TABLE 8-2  
Function Table for ALU

Operation Select				Operation	Function
S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	C <sub>in</sub>		
0	0	0	0	$G = A$	Transfer $A$
0	0	0	1	$G = A + 1$	Increment $A$
0	0	1	0	$G = A + B$	Addition
0	0	1	1	$G = A + B + 1$	Add with carry input of 1
0	1	0	0	$G = A + \overline{B}$	$A$ plus 1s complement of $B$
0	1	0	1	$G = A + \overline{B} + 1$	Subtraction
0	1	1	0	$G = A - 1$	Decrement $A$
0	1	1	1	$G = A$	Transfer $A$
1	X	0	0	$G = A \wedge B$	AND
1	X	0	1	$G = A \vee B$	OR
1	X	1	0	$G = A \oplus B$	XOR
1	X	1	1	$G = \overline{A}$	NOT (1s complement)

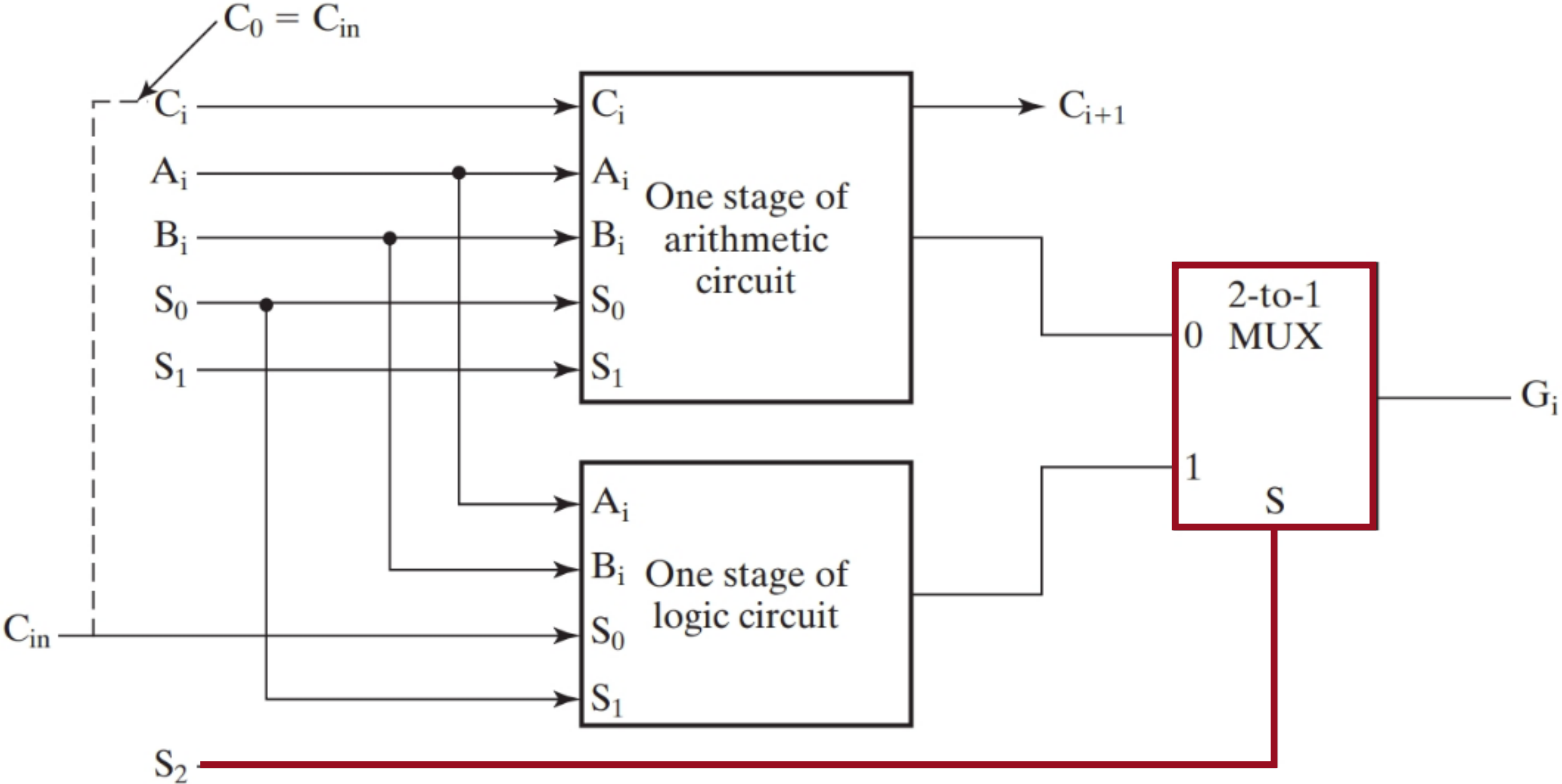


FIGURE 8-7  
One Stage of ALU


Selection input S1 has no effect during the logic operations and is marked with X to indicate that its value may be either 0 or 1




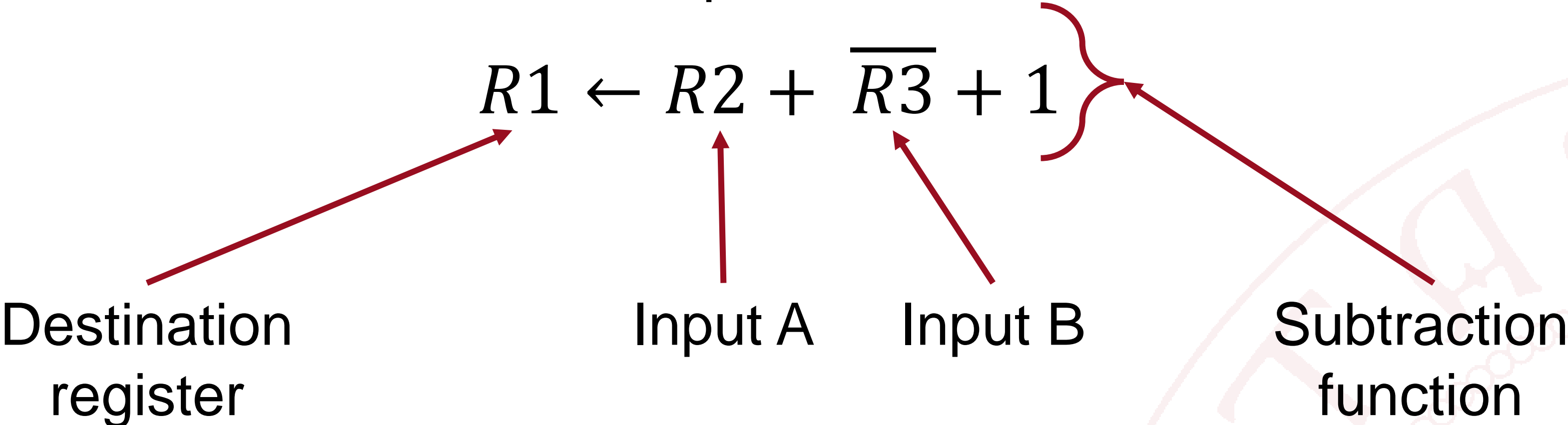
# Examples of control word (1)

The control word for a given microoperation can be deriving by specifying the value of each of the control fields. For example:



Field:	DA	AA	BA	MB	FS	MD	RW
Symbolic:	R1	R2	R3	Register	$F = A + \overline{B} + 1$	Function	Write
Binary:	001	010	011	0	0101	0	1

DA			AA			BA			MB	FS				MD	RW
0	0	1	0	1	0	0	1	1	0	0	1	0	1	0	1

control word





# Examples of control word (2)

□ TABLE 8-6

Examples of Microoperations for the Datapath, Using Symbolic Notation

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 - R3$	$R1$	$R2$	$R3$	Register	$F = A + \overline{B} + I$	Function	Write
$R4 \leftarrow \text{sl } R6$	$R4$	—	$R6$	Register	$F = \text{sl } B$	Function	Write
$R7 \leftarrow R7 + 1$	$R7$	$R7$	—	—	$F = A + 1$	Function	Write
$R1 \leftarrow R0 + 2$	$R1$	$R0$	—	Constant	$F = A + B$	Function	Write
$\text{Data out} \leftarrow R3$	—	—	$R3$	Register	—	—	No Write
$R4 \leftarrow \text{Data in}$	$R4$	—	—	—	—	Data in	Write
$R5 \leftarrow 0$	$R5$	$R0$	$R0$	Register	$F = A \oplus B$	Function	Write

# Examples of control word (3)

□ **TABLE 8-7**

**Examples of Microoperations from Table 8-6, Using Binary Control Words**

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 - R3$							
$R4 \leftarrow sl\ R6$							
$R7 \leftarrow R7 + 1$							
$R1 \leftarrow R0 + 2$							
Data out $\leftarrow R3$							
$R4 \leftarrow \text{Data in}$							
$R5 \leftarrow 0$							



# Sequence of microoperations

Assumptions:

- The number of bit in each register is equal to 8
- An unsigned decimal representation is used for all multiplebit signals
- The microoperations are executed in sequence:

TABLE 8-7  
Examples of Microoperations from Table 8-6, Using Binary Control Words

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 - R3$	001	010	011	0	0101	0	1
$R4 \leftarrow sl\ R6$	100	XXX	110	0	1110	0	1
$R7 \leftarrow R7 + 1$	111	111	XXX	X	0001	0	1
$R1 \leftarrow R0 + 2$	001	000	XXX	1	0010	0	1
$Data\ out \leftarrow R3$	XXX	XXX	011	0	XXXX	X	0
$R4 \leftarrow Data\ in$	100	XXX	XXX	X	XXXX	1	1
$R5 \leftarrow 0$	101	000	000	0	1010	0	1

The result of the subtraction in clock cycle 1 appears in register R1 in clock cycle 2

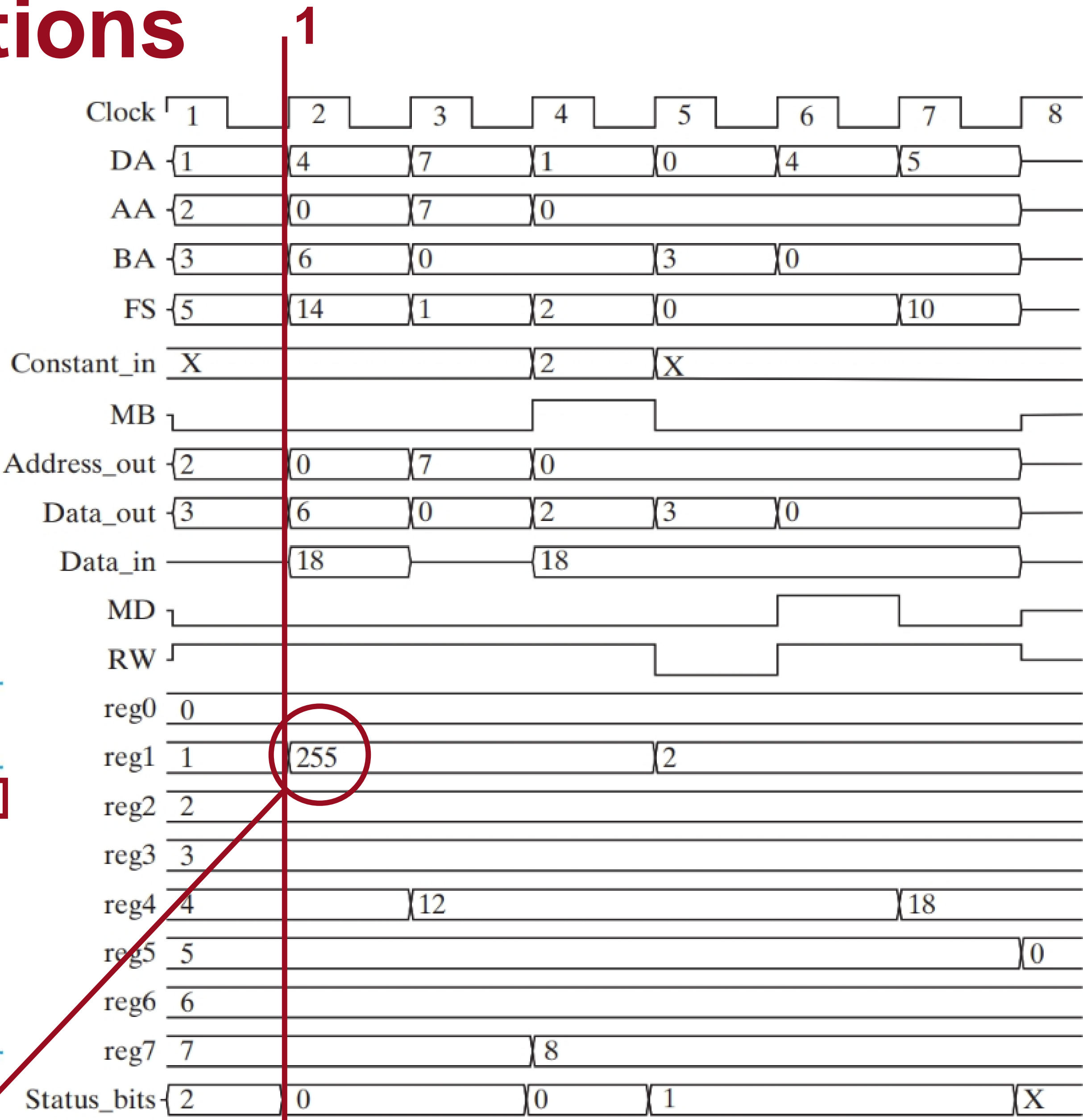


FIGURE 8-12  
Simulation of the Microoperation Sequence in Table 8-7

# Sequence of microoperations

Assumptions:

- The number of bit in each register is equal to 8
- An unsigned decimal representation is used for all multiplebit signals
- The microoperations are executed in sequence:

TABLE 8-7  
Examples of Microoperations from Table 8-6, Using Binary Control Words

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 - R3$	001	010	011	0	0101	0	1
$R4 \leftarrow sl\ R6$	100	XXX	110	0	1110	0	1
$R7 \leftarrow R7 + 1$	111	111	XXX	X	0001	0	1
$R1 \leftarrow R0 + 2$	001	000	XXX	1	0010	0	1
$Data\ out \leftarrow R3$	XXX	XXX	011	0	XXXX	X	0
$R4 \leftarrow Data\ in$	100	XXX	XXX	X	XXXX	1	1
$R5 \leftarrow 0$	101	000	000	0	1010	0	1

Result available in R4  
at the next clock cycle

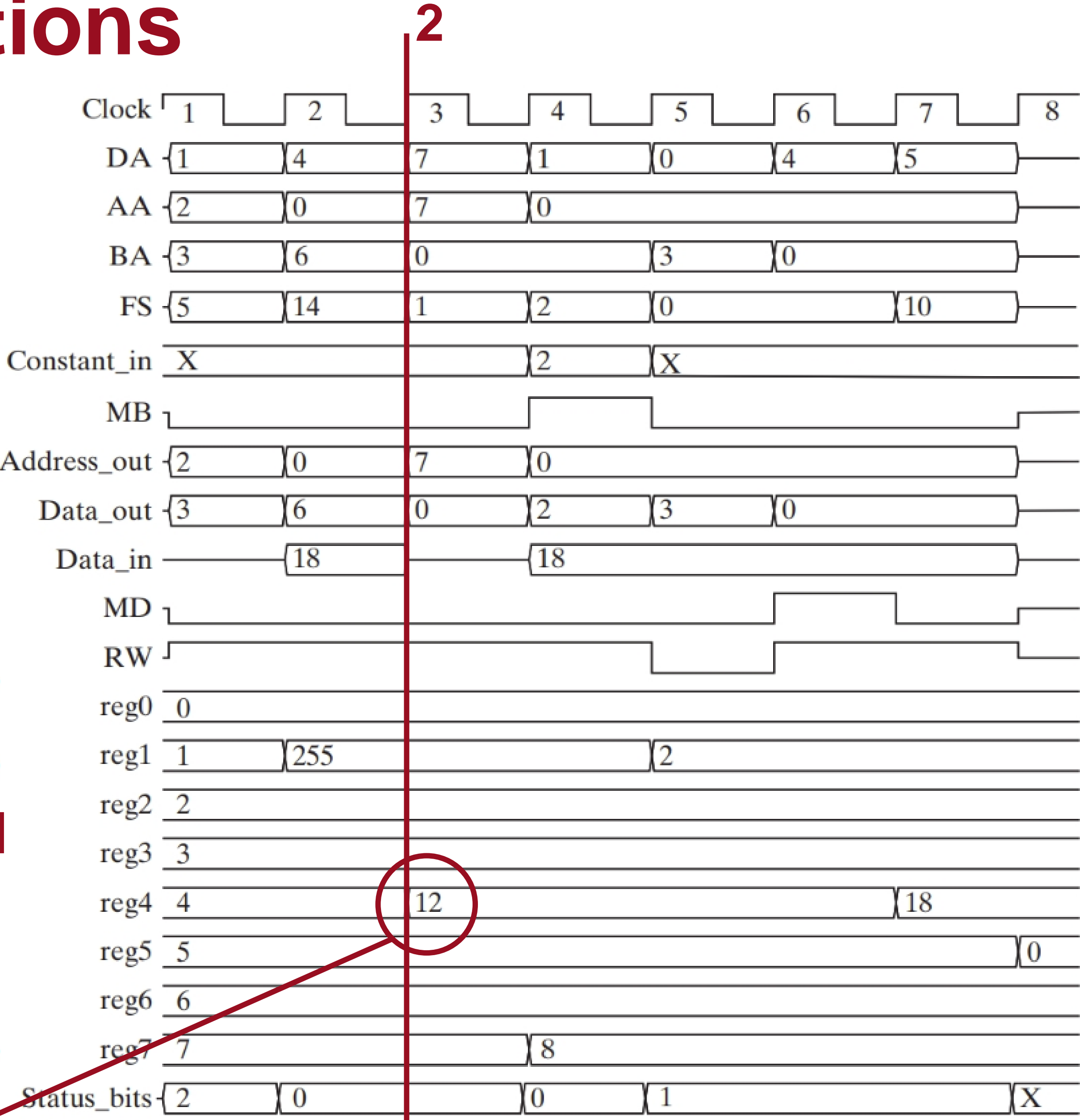


FIGURE 8-12  
Simulation of the Microoperation Sequence in Table 8-7



# Sequence of microoperations

Assumptions:

- The number of bit in each register is equal to 8
- An unsigned decimal representation is used for all multiplebit signals
- The microoperations are executed in sequence:

TABLE 8-7  
Examples of Microoperations from Table 8-6, Using Binary Control Words

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 - R3$	001	010	011	0	0101	0	1
$R4 \leftarrow \text{sl } R6$	100	XXX	110	0	1110	0	1
$R7 \leftarrow R7 + 1$	111	111	XXX	X	0001	0	1
$R1 \leftarrow R0 + 2$	001	000	XXX	1	0010	0	1
$\text{Data out} \leftarrow R3$	XXX	XXX	011	0	XXXX	X	0
$R4 \leftarrow \text{Data in}$	100	XXX	XXX	X	XXXX	1	1
$R5 \leftarrow 0$	101	000	000	0	1010	0	1

Result available in R7  
at the next clock cycle


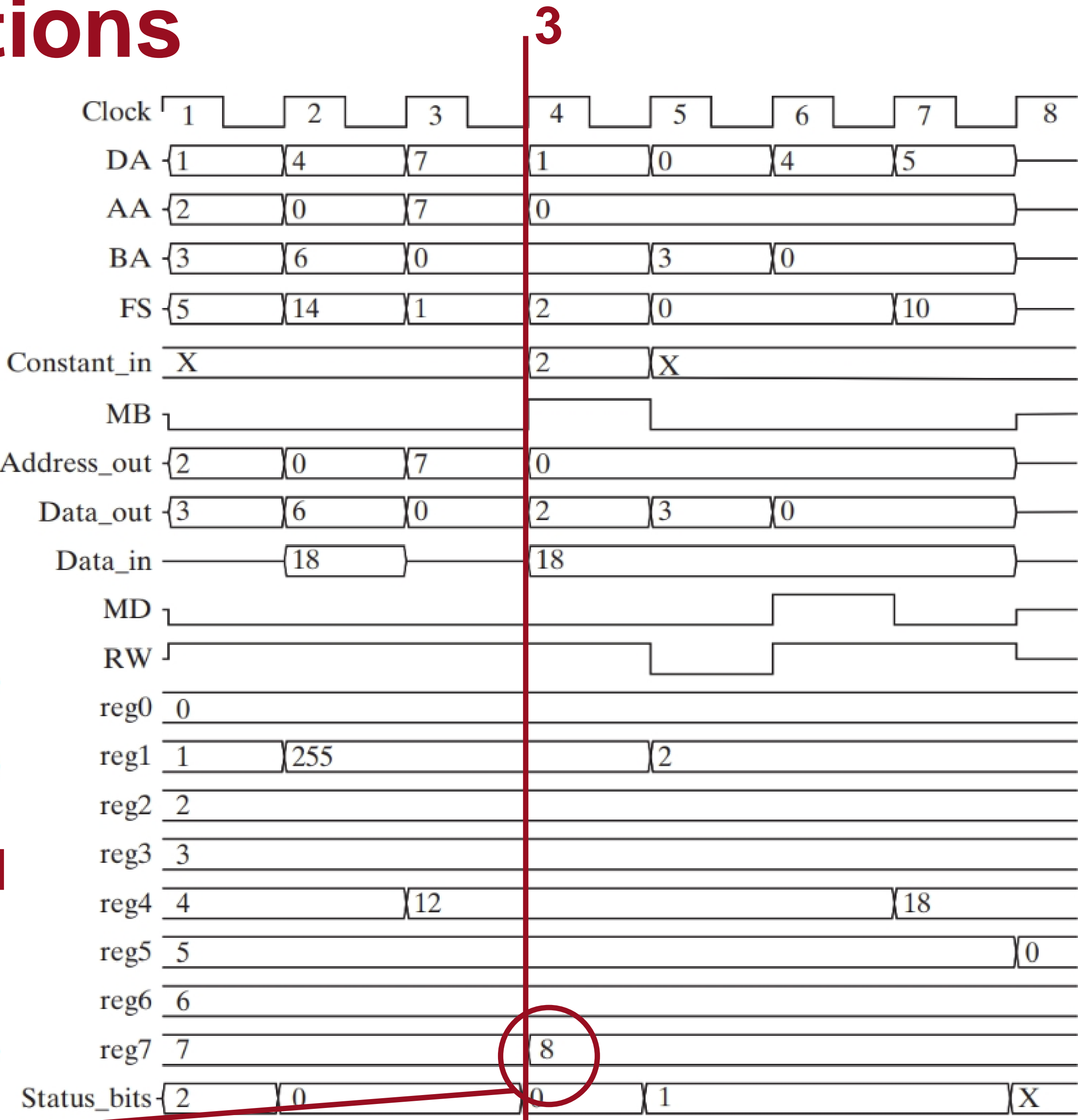


FIGURE 8-12  
Simulation of the Microoperation Sequence in Table 8-7
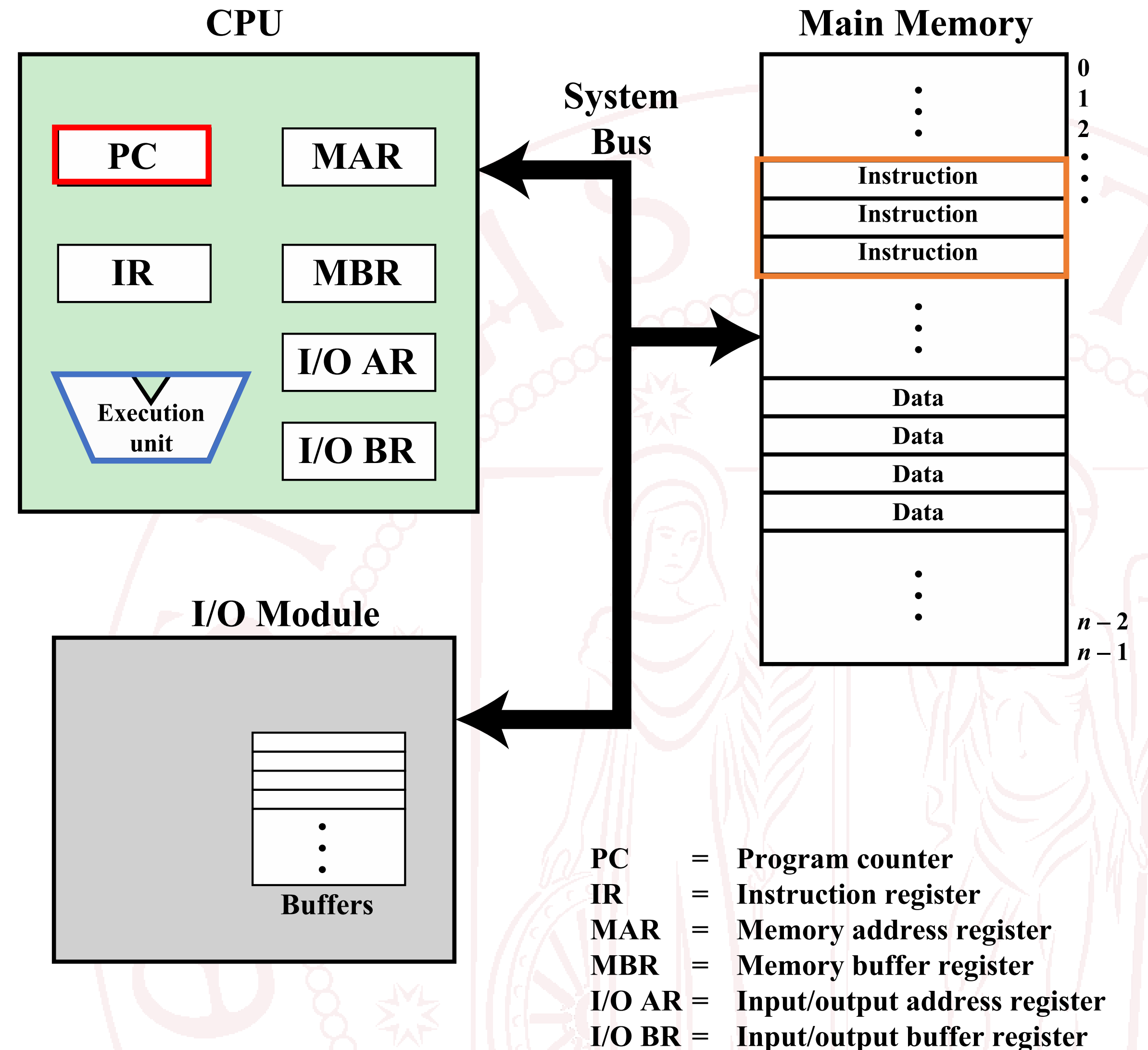
# Instructions and e microoperations

- In a programmable system, a portion of the input to the processor consists of a **sequence of instructions**
- **Each instruction specifies:**
  - an operation the system has to perform
  - which operands to use
  - where to place the results
  - (which instruction to execute next)
- The **instructions** are usually stored in memory and they are loaded in sequence into registers.
- To execute the instructions in sequence, the register called **Program Counter (PC)** provides the address in memory of the instruction to be executed
- A program is a list of instructions






# Instruction Set Architecture (ISA)

- An *instruction* is a collection of bits that instructs the computer to perform a specific operation.
- The collection of instructions for a computer is called **Instruction Set**
- A detailed description of the instruction set provides an abstract model of the computer that is called **Instruction Set Architecture (ISA)**
- The simplest ISA has three major components:
  - Storage resources
  - Instruction formats
  - Instruction specifications

# Storage resources
 
## Resource available to the programmer:

- **Instruction memory:** where the instructions are stored
- **Data memory:** where data are stored
- **Register file:** registers where the data are saved inside the processor
- **Program counter:** provides the address in memory of the instruction to be executed




□ **FIGURE 8-13**  
Storage Resource Diagram for a Simple Computer



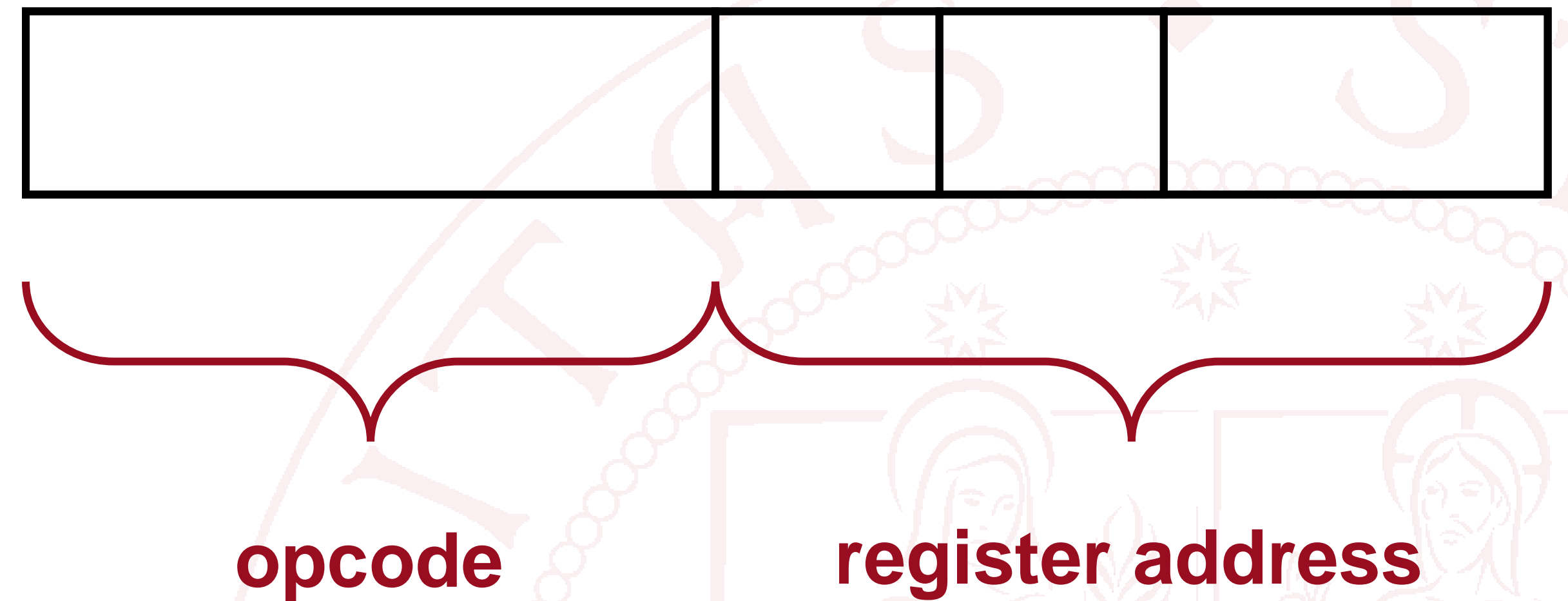
# Instruction formats

- The format of an instruction is usually depicted by a rectangular box symbolizing the bits of the instruction
- The representation of the bits is as they appear in memory words or in a control register
- The instruction is divided into fields that specify:
  - The operation code (opcode)
  - Register file address


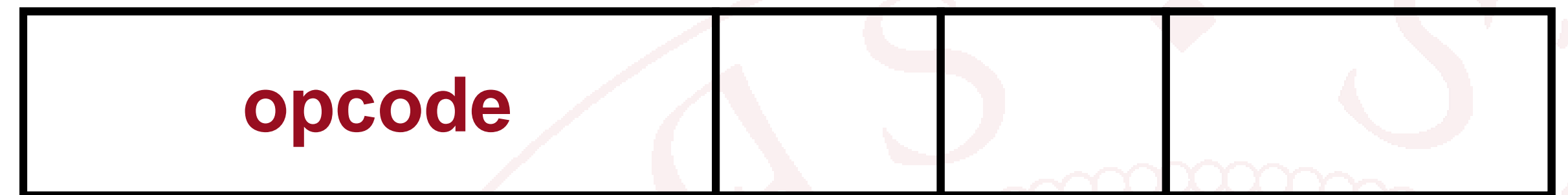
# Instruction formats: operation code (opcode)

- The opcode is a group of bits in the instruction that specifies the operation to be performed (e.g., add, sub, shift..)
- The number of bits required for the opcode of an instruction depends on the total number of distinct operations in the instruction set ( $m$  bits for up to  $2^m$  distinct operations)
- The designer assigns a bit combination (code) to each operation.



For example:

- Processor with 128 distinct operations
- $2^m = 128 \rightarrow m = 7 \rightarrow$  opcode with 7 bit
- opcode: 0000010
- When the opcode is detected by the control unit, a sequence of control words is applied to the datapath



# Instruction formats: register addresses, operands

- The operation must be performed using data stored in computer registers or in a memory
- An instruction, therefore, must specify not only the operation, but also the **operands** and where the **result** has to be placed
- The operands may be specified in two ways:
  - **explicitly**, if the instruction contains special bits for its identification
  - **implicitly**, if it is included as a part of the definition of the operation itself (represented by the opcode)



## Explicit operands

For instance, the instruction performing an addition ( $R1 \leftarrow A + B$ ) may contain:

- 2 registers for the two operands ( $A, B$ )
- 1 register for the result ( $R1$ )


## Implicit operands

For instance, in an Increment Register operation ( $R7 \leftarrow R7 + 1$ ), one of the operands is *implicitly*  $+ 1$

# Disclaimer

Figures from *Logic and Computer Design Fundamentals*,  
Fifth Edition, GE Mano | Kime | Martin

© 2016 Pearson Education, Ltd

 



# Questions

